





Correction of SW Series N° 04

ELECTRO-KINETICS


Exercise 1

1- To calculate the equivalent resistance, simplify the circuit:

$$R_{eq1} = 16 + 4 + 4 = 24 \Omega$$

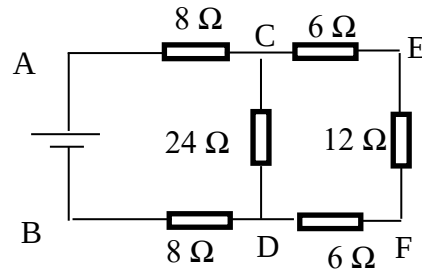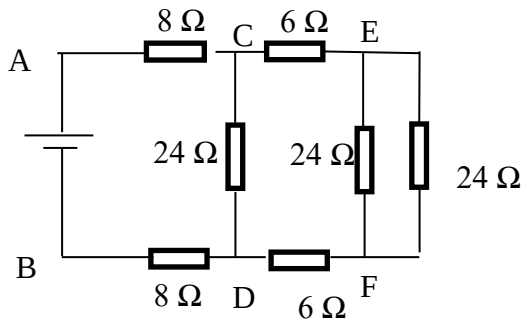


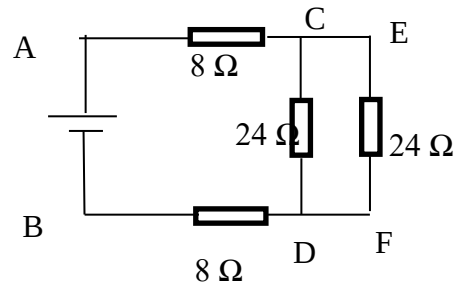Then $\frac{1}{R_{eq2}} = \frac{1}{24} + \frac{1}{24} = \frac{2}{24} = \frac{1}{12}$
So $R_{eq2} = 12 \Omega$



$$R_{eq3} = 12 + 6 + 6 = 24 \Omega$$
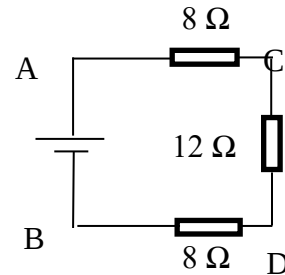
$$\frac{1}{R_{eq4}} = \frac{1}{24} + \frac{1}{24} = \frac{2}{24} = \frac{1}{12} \text{ so } R_{eq4} = 12 \Omega$$




So
 $R_{eq} = 8 + 8 + 12 = 28 \Omega$

2- The intensity I of the current delivered by the generator, specifying the direction of flow:

$$E = R_{eq} I \Rightarrow I = \frac{E}{R_{eq}}$$

$$\text{So } I = \frac{56}{28} = 2A$$

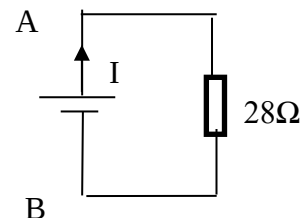

3- the potentiel $V_{AC} = R_{AC} I = 8 \times 2 = 16V$


The current flowing in the CD branch

In the ACDBA Loop (in this direction)

$$E - V_{AC} - V_{CD} - V_{DB} = 0$$

$$\Rightarrow E - 8I - 24I_1 - 8I = 0$$
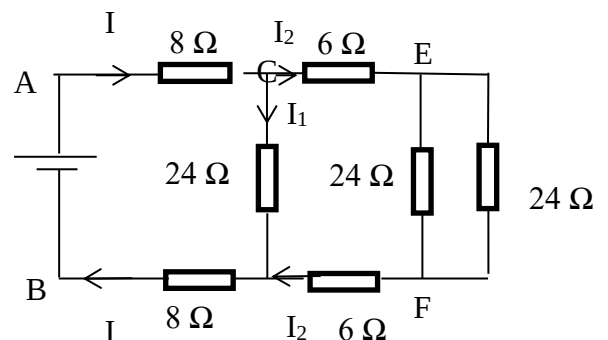
$$I_1 = \frac{E - 16I}{24} = \frac{56 - 32}{24} = 1A$$



4- V_{EF} voltage between points E and F

In the CCLD Loop (in this direction).



$$V_{DC} - V_{CE} - V_{EF} - V_{FD} = 0 \Rightarrow V_{EF} = V_{DC} - V_{CE} - V_{FD}$$

$$\Rightarrow V_{EF} = 24I_1 - 6I_2 - 6I_2$$

$$I_2 = I - I_1 = 2 - 1 = 1A$$

$$V_{EF} = 24 - 12 = 12V$$

The current flowing through the EF

$$V_{EF} = R_{EF} I_{EF} \Rightarrow I_{EF} = \frac{V_{EF}}{R_{EF}} = \frac{12}{24} = 0.5A$$

2. Calculate the voltage V_{GH} between points G and H, and deduce the current in the branche GH.

$$V_{EF} = V_{EG} + V_{GH} + V_{HF} = (4 + 16 + 4)I' \text{ so } I' = 12/24 = 0.5A$$

$$\text{Then } V_{GH} = 0.5 * 16 = 8V$$

3. Power dissipated by the generator:

$$P = EI = 56V \times 2mA = 112mW$$

Exercise 2 :

1- Calculation of currents I_2 et I_3 : (figure 3)

$$\text{Loop 1 : } R_1 I_1 = 0 \Rightarrow I_1 = 0$$

$$\text{Loop 2 : } R_2 I_2 - E = 0 \Rightarrow I_2 = 1A$$

$$\text{Loop 3 : } R_3 I_3 - E = 0 \Rightarrow I_3 = 3A$$

Calculation of generator output current:

$$\text{Node C we have : } I_2 + I_3 = I_e = 4A$$

2- Calculation of currents I_1 , I_2 et I_3 : (figure 4)

$$\text{Node A: } I_1 = I_2 + I_3$$

$$\text{Loop 1: } E - R_1 I_1 - R_2 I_2 = 0$$

$$\text{Loop 2: } R_2 I_2 - R_3 I_3 = 0$$

$$I_1 = \frac{E - R_2 I_2}{R_1} = 4(1 - I_2)$$



$$\text{and } I_3 = \frac{R_2 I_2}{R_3} = 3I_2 \text{ so } 4(1 - I_2) = I_2 + 3I_2$$

$$I_2 = 0.5A \text{ and } I_1 = 2A \text{ so } I_3 = 3I_2 = 1.5A$$

3- Find I_1 using R_{eq} :

$$R_{eq} = R_1 + (R_2 * R_3) / (R_2 + R_3) = 60\Omega$$

$$\text{We have } E = R_{eq} I_1 \text{ so } I_1 = E / R_{eq} = 120/60 = 2A$$

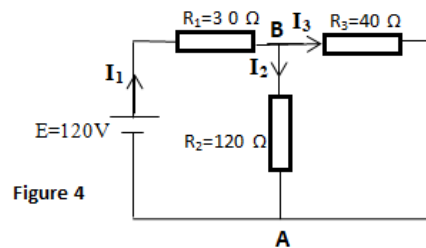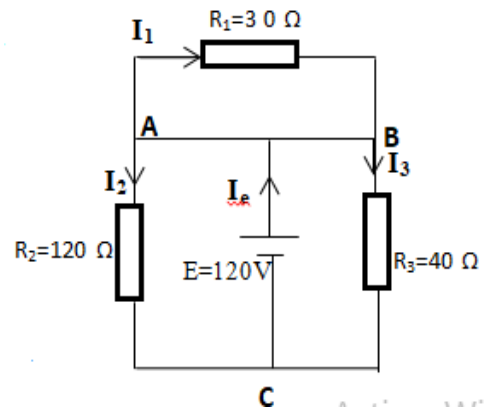

Exercise 3:

The current intensity I using


Kirchoff's laws :

- Law of nodes : $I_1 = I_2 + I_3$

Law of loop:

$$E - R_1 I_1 - R_2 I_2 = 0$$

$$R_2 I_2 - R_3 I_3 - R_{45} I_3 = 0$$

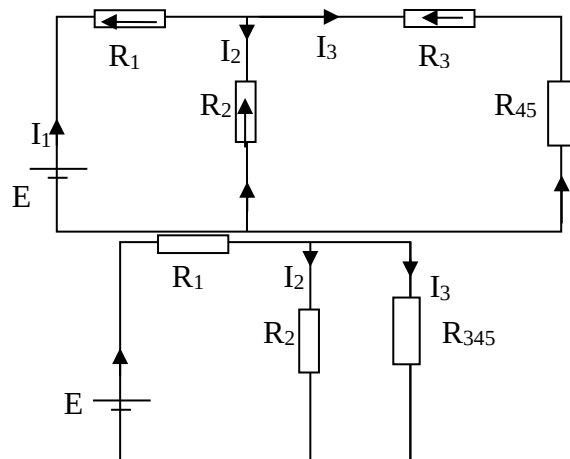




$$\frac{1}{R_{45}} = \frac{1}{R_4} + \frac{1}{R_5} = \frac{1}{6} + \frac{1}{12} = \frac{3}{12} \Rightarrow R_{45} = 4\Omega$$

$$\begin{cases} 12 - 2I_1 - 20I_2 = 0 \\ 20I_2 - 16I_3 - 4I_3 = 0 \\ I_1 = I_2 + I_3 \end{cases}$$
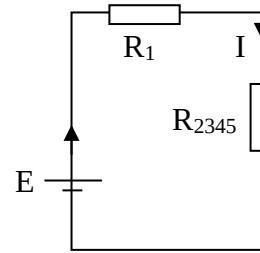
$$\Rightarrow \begin{cases} 12 - 2(I_2 + I_3) - 20I_2 = 0 \\ 20I_2 - 16I_3 - 4I_3 = 0 \end{cases} \Rightarrow \begin{cases} 12 - 2I_3 - 22I_2 = 0 \\ 20I_2 - 20I_3 = 0 \end{cases}$$




$$I_2 = I_3 \text{ so } 12 - 24I_2 = 0 \text{ Then } I_2 = I_3 = 0,5 \text{ A and } I_1 = 1 \text{ A}$$

2- The current I using the equivalent resistance:

$$R_{345} = 16 + 4 = 20\Omega, \frac{1}{R_{2345}} = \frac{1}{R_2} + \frac{1}{R_{345}} = \frac{1}{20} + \frac{1}{20} = \frac{2}{20} \Rightarrow R_{2345} = 10\Omega$$
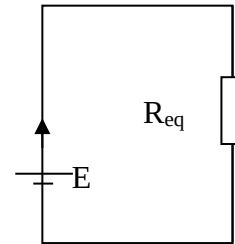
$$R_{eq} = R_1 + R_{2345} = 2 + 10 = 12\Omega \text{ with } E - R_{eq}I_1 = 0 \text{ so } I_1 = \frac{E}{R_{eq}} = \frac{12}{12} = 1 \text{ A}$$



2- The ddp to the R_2 : $U_2 = R_2 I_2 = 20 \times 0,5 = 10 \text{ V}$

3- The power generated by R_2 : $P_2 = R_2 (I_2)^2 = U_2 \times I_2 = 10 \times 0,5 = 5 \text{ W}$

4- Circulating currents in resistances R_4 and R_5

$$U_{45} = R_{45} I_3 = 4 \times 0,5 = 2 \text{ V with } U_{45} = U_4 = U_5 \Rightarrow U_{45} = R_4 I'_3 = R_5 I''_3$$

$$\text{So } I'_3 = \frac{U_{45}}{R_4} = \frac{2}{6} = \frac{1}{3} \text{ A and } I''_3 = \frac{U_{45}}{R_5} = \frac{2}{12} = \frac{1}{6} \text{ A}$$


Exercise 4 :

$$U_{R2} = R_2 I_2 \text{ so } I_2 = U_{R2} / R_2 = 8 \text{ V} / 2 \text{ k}\Omega = 4 \text{ mA}$$

$$U_{R3} = R_3 I_2 = 4 \text{ k}\Omega \times 4 \text{ mA} = 16 \text{ V}$$

$$U_{AB} = U_{R2} + U_{R3} = 8 + 16 = 24 \text{ V}$$
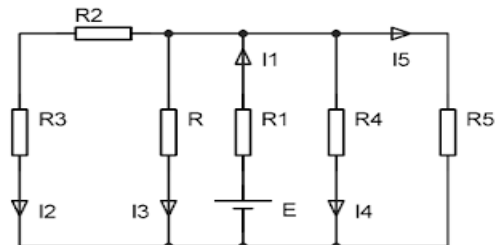
$$U_{AB} = R I_3 \text{ so } R = U_{AB} / I_3 = 24 \text{ V} / 2 \text{ mA}$$



Then $R = 12 \text{ k}\Omega$

$$U_{AB} = U_{R4} = U_{R5} = 24 \text{ V et } R_4 = R_5 \text{ and } I_4 = I_5 = U_{AB} / R_4 \text{ with } I_4 = I_5 = 24 \text{ V} / 3 \text{ k}\Omega = 8 \text{ mA}$$

We apply the law of knots to the point A :

$$I_1 = I_2 + I_3 + I_4 + I_5 = 2 \text{ mA} + 4 \text{ mA} + 8 \text{ mA} + 8 \text{ mA} = 22 \text{ mA}$$


$$U_{AB} = E - R_1 I_1 \text{ so } E = U_{AB} + R_1 I_1$$

$$E = 24 \text{ V} + 1 \text{ k}\Omega \times 22 \text{ mA} \text{ then } E = 46 \text{ V}$$



Exercise 5 :

Circuit simplification:

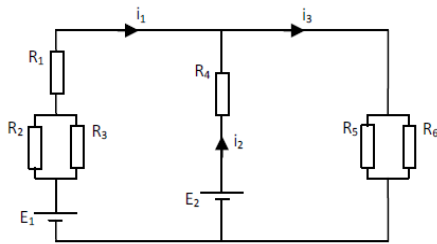

$$\frac{1}{R_{23}} = \frac{1}{20} + \frac{1}{20} = \frac{1}{10} \Rightarrow R_{23} = 10\Omega,$$

and $R_{123}=10+10=20\Omega$,

$$\frac{1}{R_{56}} = \frac{1}{6} + \frac{1}{3} = \frac{3}{6} \Rightarrow R_{56} = 2\Omega$$

In this circuit, we have two generators: E_1 and E_2 .

E_1 is a generator because it gives the current I_1 , E_2 is also a generator, it gives the current I_2 .

2- The currents I_1 , I_2 et I_3

Law of nodes: $I_1 + I_2 = I_3$

Law of loops :

$$E_1 - R_{123}I_1 - R_4I_2 - E_2 = 0 \Rightarrow 20 - 20I_1 - 10I_2 - 10 = 10 - 20I_1 - 10I_2 = 0 \quad (1)$$

$$E_2 - R_4I_2 - R_{56}I_3 = 0 \Rightarrow 10 - 5I_2 - 2I_3 = 0$$

$$10 - 5I_2 - 2(I_1 + I_2) = 10 - 2I_1 - 7I_2 = 0$$

$$10 - 2I_1 - 7I_2 = 0 \quad (2)$$

We do $(1) - 10 \times (2)$ we will have $(10 - 20I_1 - 10I_2) - (100 - 20I_1 - 70I_2) = -90 + 60I_2 = 0$


$$(1) - 10 \times (2) = -90 + 60I_2 = 0 \Rightarrow I_2 = 1.5A, \text{ and } (2) \Rightarrow 10 - 2I_1 - 10.5 = -0.5 - 2I_1 = 0 \text{ so } I_1 = -0.25A$$

$$\text{And } I_3 = 1.5 - 0.25 = 1.25A$$

Additional exercise

1- Assuming the capacitor is fully charged, calculate the currents I_1 , I_2 and I_3 .

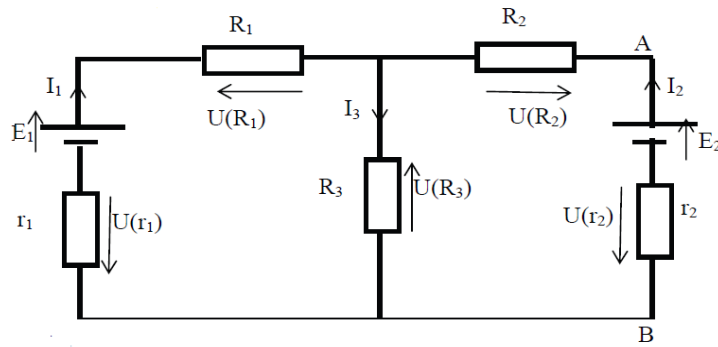Since the capacitor is fully charged, the current does not flow, so the circuit will be as follows:



Law of nodes $I_3 = I_1 + I_2$

According to the law of loops:

$$E_1 - R_1 I_1 + R_2 I_2 - E_2 + r_2 I_2 - r_1 I_1 = 0$$

$$E_1 - R_1 I_1 - R_3 I_3 - r_1 I_1 = 0 \quad \text{so} \quad E_1 - R_1 I_1 - R_3 I_1 - R_3 I_2 - r_1 I_1 = 0$$

By replacing I_3 with $I_1 + I_2$, we will have:

$$E_1 - (R_1 + R_3 + r_1) I_1 - R_3 I_2 = 0$$

$$E_2 - (R_2 + R_3 + r_2) I_2 - R_3 I_1 = 0$$

$$E_1 = 12\text{V}, E_2 = 8\text{V}, r_1 = r_2 = 1\Omega, R_1 = 4\Omega, R_2 = 3\Omega, R_3 = 5\Omega$$

$$12 - 10 I_1 - 5 I_2 = 0$$

$$(8 - 5 I_1 - 9 I_2 = 0) \times 2 \Rightarrow 16 - 10 I_1 - 18 I_2 = 0$$

$$-4 + 12 I_2 = 0 \quad \text{so} \quad I_2 = 0,3 \text{ A}$$

$$10 I_1 + 5 I_2 - 12 = 0 \quad (1)$$

$$5 I_1 + 9 I_2 - 8 = 0 \quad (2)$$

$$\text{In doing so : } (1) - 2 \times (2) = 4 - 13 I_2 = 0$$


We then find : $I_2 = 0.3 \text{ A}$, $I_1 = 1.05 \text{ A}$ and $I_3 = 1.35 \text{ A}$

2- The difference in potential between A and B

$$U_{AB} = V_A - V_B = E_2 - r_2 I_2 = 7.7 \text{ V}$$

3- Capacitor charge Q_C

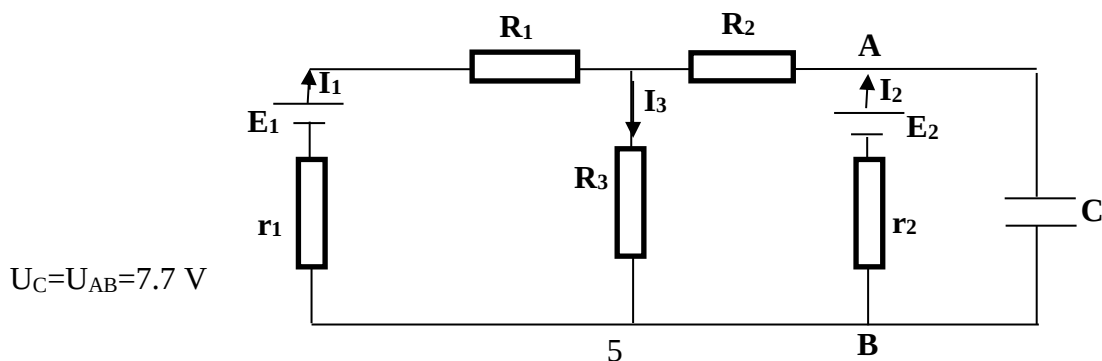Find the potential difference across the capacitor:





The charge Q_C

$$Q_C = C U_C = 2 \times 7.7 \times 10^{-6} = 1.54 \mu C$$

The energy stored in the capacitor is :

$$E_C = \frac{1}{2} (C U^2) = \frac{1}{2} (2 \times 10^{-6}) (7.7)^2 = 59.29 \times 10^{-6} \text{ joule}$$

4- The power generated by R_3

$$P = U_3 I_3 = R_3 I_3^2 = 5 \times (1.35)^2 = 9.112 \text{ Watt}$$