

الجمهورية الجزائرية الديمقراطية الشعبية
REPUBLIQUE ALGERIENNE DEMOCRATIQUE ET POPULAIRE
وزارة التعليم العالي و البحث العلمي
Ministère de l'Enseignement Supérieur et de la Recherche Scientifique
جامعة أبي بكر بلقايد – تلمسان
Université Aboubakr Belkaïd – Tlemcen –
Faculté de TECHNOLOGIE



Biomedical Engineering Department

1st year Common Core in biomedical Engineering

Tutorials on Electrical Circuits

by :

- Radhwane BENALI

Co-authors :

- Nabil DIB

- Salim KERALI

Preface

This handout is a learning guide for first-year Biomedical Engineering students at Abou Bekr Belkaid University, Tlemcen. It covers the fundamental principles of electrical circuits, which are essential for future studies in biomedical engineering.

This document serves as a supplement to the “**Electrical Circuits**” courses, offering additional exercises to enhance understanding. It includes comprehensive course notes, a variety of exercises with detailed solutions, and engaging homework assignments.

We extend our gratitude to **Debbal Sidi Mohammed** and **Habibes Naima** for their careful review and corrections, ensuring the accuracy of this work.

We wish you success in your studies and hope this resource helps you master electrical circuits.

Table of Contents

Tutorial 1 : Charge, Current, Energy & voltage

Tutorial 2 : Combining Resistors, Kennelly theorem, Ohm's law, Power balance

Tutorial 3 : Kirchhoff rules

Tutorial 4 : Voltage divider / Current divider

Tutorial 5 : Superposition theorem

Tutorial 6 : Thevenin theorem

Tutorial 7 : Norton theorem

Tutorial 8 : Millman theorem

Bibliography

Tutorial 1

Course Notes: Charge, Current, Energy & voltage

Charge, Current

- Charge, symbolized by Q and measured in coulombs, serves as an attractive force [1].
- Electrons bear a negative charge, while protons are positively charged, both exhibiting a charge magnitude of approximately 1.602×10^{-19} coulombs.
- This implies that one coulomb equals the charge carried by roughly 6.242×10^{18} electrons.
- The opposite charges attract but the like charges repel [3].
- Charge can be transferred, and the rate of this movement is termed current, denoted by I in amperes.
- One ampere equals one coulomb per second, or about 6.242×10^{18} electrons will pass over a wire in 1 second [2].

Current I

Electrical current I represent the flow of the electric charges in a conductor. The unit is amperes (A).

It means the rate at which the electric charges passes through the conductor.

The formula is:

$$I = Q/t$$

I : current (A)
Q : charge (C)
t : time (s)

Example

A battery delivers 4 coulombs of charge in half a second. What is the current?

Solution

$$I = Q / t = 4 / 0.5 = 4 / 0.5 = 8 \text{ A}$$

Example

We have a device that delivers 50 mA. Calculate the charge moved in 2 seconds and the total number of electrons involved.

Solution

1) Charge : $Q = I * t = 50 \text{ (mA)} * 2 \text{ (s)} = 100 \text{ mC} = 0,1 \text{ C}$

2) $1 \text{ C} = 6.242 \cdot 10^{18}$ electrons, so the equivalent electrons = $Q * 6.242 \cdot 10^{18}$

Equivalent of electrons = $100 * 6.242 \cdot 10^{18} = 6.242 \cdot 10^{17}$ electrons

Energy & Voltage

- Energy, denoted as E and measured in joules (J), represents the capacity to perform work.
- Moving a charge, like separating an electron from an atom, requires energy.
- This energy is reflected in the concept of electric potential difference, known as voltage.
- Voltage V is measured in volts (v).

$$V = E/Q$$

V : voltage (v)

E : Energy (J)

Q : Charge (C)

Unlike current, voltage always involves a difference between two points with a reference point like earth ground.

For example, V_{AB} indicates the voltage difference between points A and B.

$$V_{AB} = V_A - V_B$$

Example

A charge of 50 coulombs is moved from the point A to B requiring 150 joules of energy. Calculate the voltage between A and B.

Solution

Since the charge is moved from point A to point B, the potential at B is higher than A.

As a result, the voltage, which is the difference in potential between the two points, is directed from B to A.

$$V_{BA} = E / Q = 150\text{J}/50\text{C} = 3\text{V}$$

Power P

Power (P) is the rate at which the energy will be consumed.

$$P = E/t$$

The formula expresses the relationship between power P (W), energy E (J), and time t (s).

Example

A device consumes 100 joules of energy in 0.2 seconds. Calculate its power consumption.

Solution

$$P = E / t = 100\text{J} / 0.2\text{s} = 500 \text{ W}$$

Power can be calculated by multiplying the current flowing through a circuit by the voltage across it.

We have : $I = Q / t$ & $V = E / Q$,

so $V * I = (E / Q) * (Q / t) = E / t = P$

$$P = V * I$$

Example

A 9-volt battery provides a current of 0.5 amperes. Calculate the power it delivers in watts.

Solution

$$P = V * I = 0.5\text{A} * 9\text{volts} = 4.5 \text{ W}$$

Homework's Assignment

Exercise No. 1

A sphygmomanometer is powered by a “6V | 1200mAh” battery. The current required for its operation is 80 mA. Calculate:

1. The duration for which the sphygmomanometer will operate.
2. The power of the sphygmomanometer.
3. The energy provided by the battery.

Exercise No. 2

A battery powers a muscle stimulator at 54 mW for 25 hours with an operating current of 12 mA. Calculate:

1. The charge of the battery.
2. The supply voltage.
3. The energy of the muscle stimulator.
4. If the operating current is 4 mA, what will be the operating duration?

Solution of Homework's Assignment

Exercise 1

According to the statements, we have : The voltage $V=6\text{v}$, the charge $Q=1200\text{ mAh}$, and the electric current is 80 mA .

- 1) The duration for which the sphygmomanometer will operate is :
 $I = Q/t$, $I=1200\text{ (mAh)}/80\text{ (mA)}$, $I=15\text{ hours}$.
- 2) The power of the sphygmomanometer is:
 $P=V.I$, $P=6 * 80.10^{-3}$, $P=0.48\text{ W}$.
- 3) Battery energy is:

$$V = E/Q, E = V*Q = 6 * 1200 * 10^{-3} * 3600 = 25920\text{ J}$$

Or

$$P = E/t, E = P * t = 0.48 * 15 * 3600 = 25920\text{ J}$$

Exercise 2

Based on the statements provided:

The power $P= 54\text{ mW}$, the time $t=25\text{ hours}$, and the electric current is 12 mA .

1. Electric Charge:

$$I = Q/t, \text{ so } Q = I * t = 12\text{ mA} * 25\text{ hours} = 300\text{ mAh}$$

$$Q = 300 (10^{-3} * 3600) = 1080\text{ Coulombs}$$

2. Supply Voltage:

$$P = V * I, \text{ so } V = P / I \Rightarrow V = 54 \times 10^{-3}\text{ W} / 12 \times 10^{-3}\text{ A}$$

$$V = 4.5\text{ V}$$

3. Energy of the Muscle Stimulator:

Method 1:

$$V = E/Q, \text{ so } E = V*Q$$

$$E = 4.5\text{V} \times 1080\text{C} \Rightarrow E = 4860\text{Joules}$$

Method 2:

$$P = E/t, \text{ so } E = P*t$$

$$E = 54 \times 10^{-3} \times 25 \times 3600 \Rightarrow E = 4860\text{Joules}$$

4. Operating Duration if $I=4\text{mA}$:

$$I = Q/t, \text{ so } t = Q/I \Rightarrow t = (1080\text{C}) / (4 \times 10^{-3})$$

$$t = 270000\text{ s}$$

$$t = 75\text{hours}$$

Problem 1

A patient is equipped with an implantable cardioverter-defibrillator (ICD). This device uses a 3.7 V, 3000 mAh lithium-ion battery. During a discharge, the ICD delivers 36 J of energy in 5 ms.





Calculate:

1. The current intensity during the discharge.
2. The voltage across the battery during the discharge (assume a constant voltage for simplicity).
3. The theoretical number of discharges the battery can provide, assuming an 80% efficiency for the conversion of chemical energy to electrical energy.
4. Estimate the battery life in years, assuming an average discharge frequency of once per month.
5. Discuss the factors that can influence the actual battery life, in addition to the discharge frequency.


Tutorial 2

Course Notes *Combining Resistors, Kennelly theorem, Ohm's law, Power balance*

Schematic symbols:

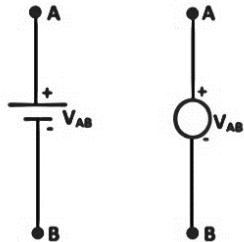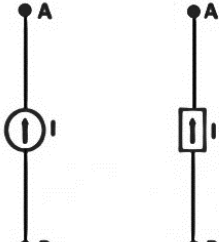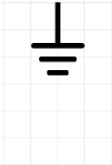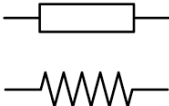Voltage source	Current source	Earth ground	Resistance
			

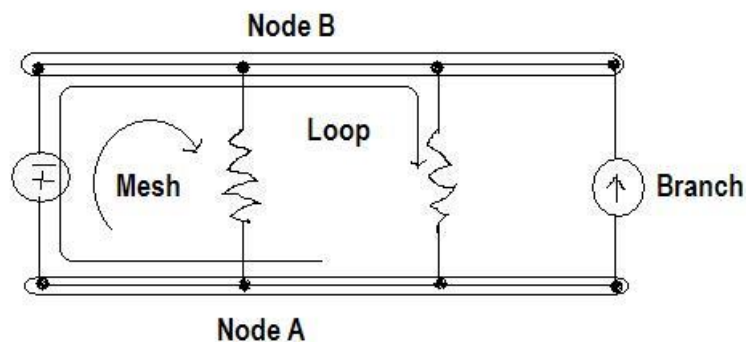To analyse electrical circuits, it's crucial to grasp key concepts like mesh, nodes and branches,



Circuit: it's a closed path through which electricity flows. It can contain various electrical components like voltage or current sources and resistors. Circuits can be simple or complex, depending on how many components they contain.

Branch: it's a single component, like a battery or resistor, with its own terminals.

Node: A node is a point where two or more branches connect.

Loop: A closed path within a circuit is a loop.


Mesh: A loop that does not have any other loops inside. All meshes are loops, but not all loops are meshes.

1) Combining Series resistors

The total resistance is found by summing the individual resistors:

$$R_{\text{Total}} = R_1 + R_2 + R_3 + \dots + R_N$$

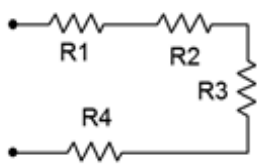Several resistors R1, R2, R3 and R4, with values of 12 ohms, 39 ohms, 56 ohms, and 47 ohms. Calculate the total resistance of this combination.



$$R = R_1 + R_2 + R_3 + R_4 = 12 + 39 + 56 + 47 = 154 \text{ ohms}$$

2) Combining Parallel resistors

The total resistance is found by :


$$1/R_{\text{parallel}} = 1/R_1 + 1/R_2 + 1/R_3 + \dots + 1/R_N$$

$$R_{\text{parallel}} = 1 / (1/R_1 + 1/R_2 + 1/R_3 + \dots + 1/R_N)$$

Simplification by using **the Product-Sum Rule** in case of 2 parallel resistors

$$R_{\text{Parallel}} = 1 / (1/R_1 + 1/R_2) = R_1 R_2 / (R_1 + R_2)$$

Calculate the R equivalent

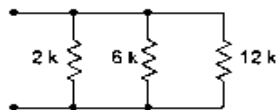


$$R = 1 / (1/2 + 1/6 + 1/12) = 1,33\text{k}$$

Or


$$R_{23} = R_2 R_3 / R_2 + R_3 = (6 * 12) / 6 + 12 = 4\text{k}$$

$$R = R_1 R_{23} / R_1 + R_{23} = (4 * 2) / 4 + 2 = 1,33\text{k}$$


Examples of Parallel network topology:

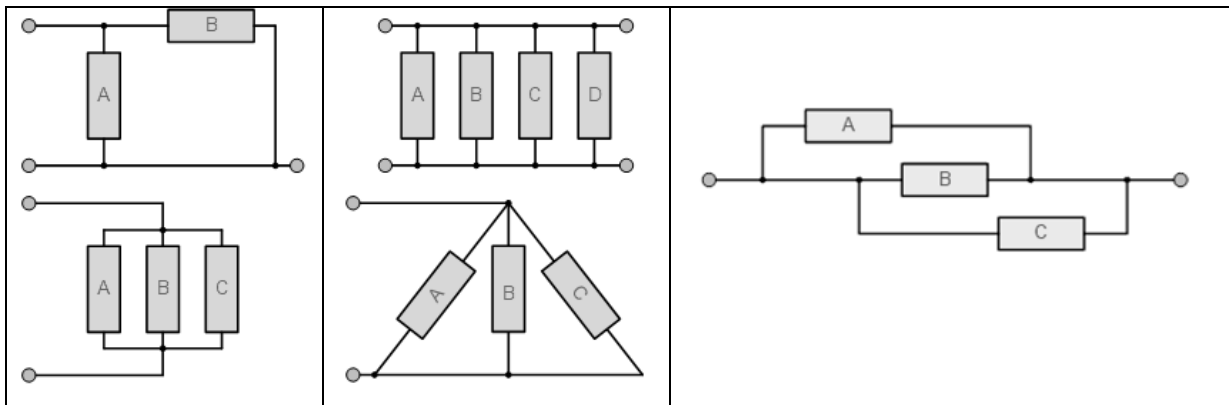

Example of simplifying a circuit

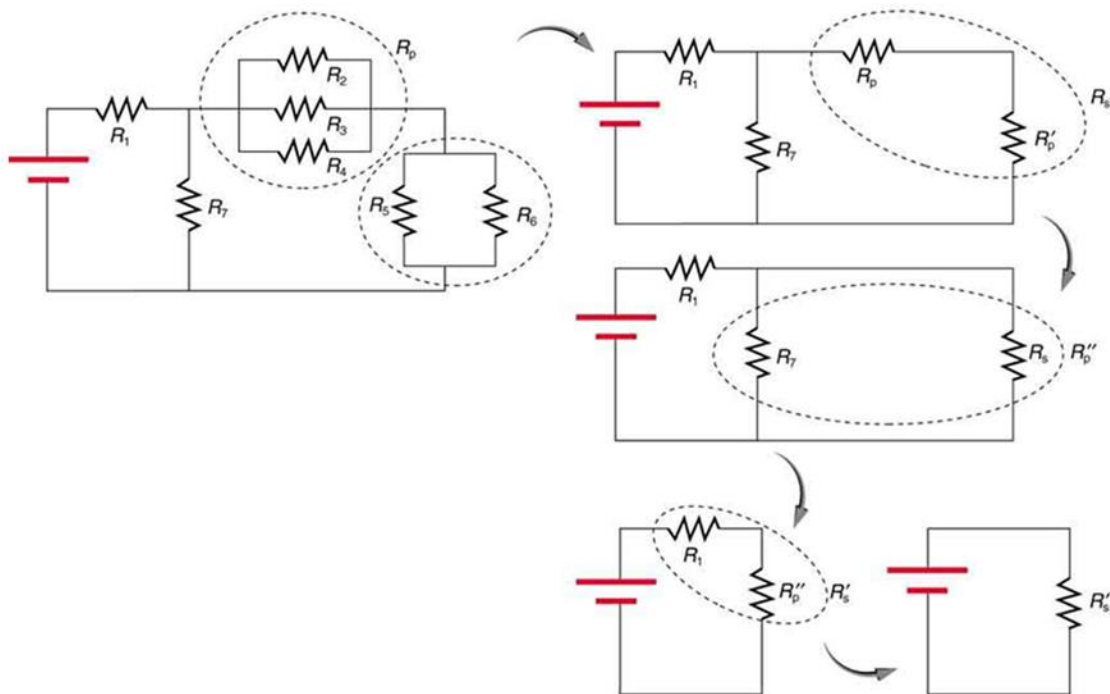

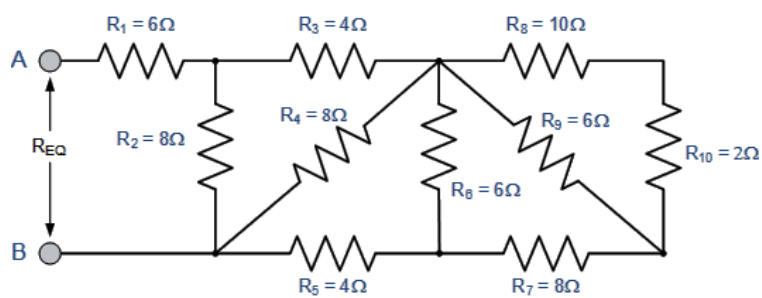
Homework's Assignment: Calculate the equivalent resistor



Result to be found: $R_{eq}=10\Omega$

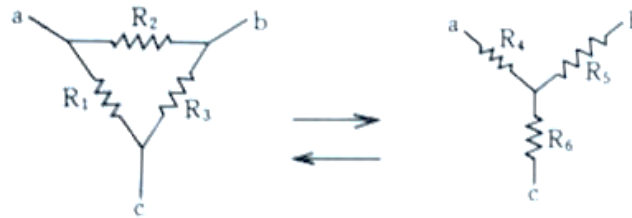3) Kennelly's theorem


Kennelly's theorem allows us to transform a circuit containing 3 resistors branched in a delta (or triangle Δ) configuration into a new configuration of 3 resistors connected in a star (or Y).




Delta to Star Transformation ($\Delta \rightarrow Y$)	Star to Delta Transformation ($Y \rightarrow \Delta$)
$R_4 = (R_1 * R_2) / (R_1 + R_2 + R_3)$ $R_5 = (R_2 * R_3) / (R_1 + R_2 + R_3)$ $R_6 = (R_1 * R_3) / (R_1 + R_2 + R_3)$	$R_1 = (R_4 * R_5 + R_5 * R_6 + R_6 * R_4) / R_5$ $R_2 = (R_4 * R_5 + R_5 * R_6 + R_6 * R_4) / R_6$ $R_3 = (R_4 * R_5 + R_5 * R_6 + R_6 * R_4) / R_4$

4) Open & short circuit

Short-circuit (closed circuit)

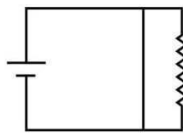

Open circuit

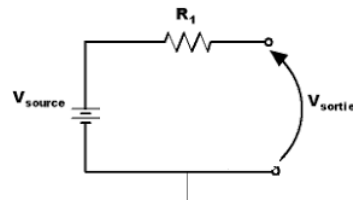


- An open circuit refers to an element with infinite resistance, resulting in the absence of electric current flow within it.
- Conversely, a short circuit represents a conductor with zero resistance, such as a conductive material.
- the case of a short circuit, the voltage across its terminals remains consistently zero

5) The rule : “Ohm's law”

$$V = R * I$$

V: voltage (volts) I: current (amperes) & R: resistance (ohms)

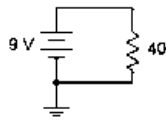A 40 ohms resistor is supplied by a 9 volts battery.
Calculate current and determine the power in the resistor.



$$P = V * I$$

$$I = V / R$$

$$P = 0,225 * 9$$

$$I = 9 / 40$$

$$P = 2,025 \text{ Watts}$$

$$= 0,225 \text{ A}$$

6) Power balance


Electrical circuits contain 2 types of components.

- **Generators:** such as batteries, direct current or alternating voltage generators, etc.
- **Receivers:** such as lamps, motors, and resistors.

The principle of power balance states that the **total power supplied** to the circuit must equal the **total power consumed** by the components within it.

$$\sum P_{generators} = \sum P_{receptors}$$

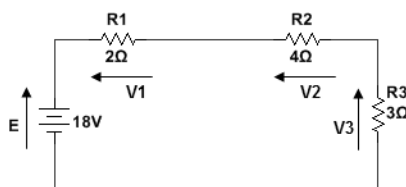Example: We aim to calculate the power distribution in this circuit



A 2A current, induced by the generator, flows through the 3 resistors.

$$P_{generator} = V * I = 18 * 2 = 36 \text{ watts}$$

$$P_{receptors} = P_{R1} + P_{R2} + P_{R3}$$

$$P_{R1} = V_1 * I = R_1 * I^2 = 2 * 4 = 8 \text{ watts}$$

$$P_{R2} = V_2 * I = R_2 * I^2 = 4 * 4 = 16 \text{ watts}$$

$$P_{R3} = V_3 * I = R_3 * I^2 = 3 * 4 = 12 \text{ watts}$$


$$\sum P_{generators} = \sum P_{receptors}$$

Exercises (Homework's Assignment)


Method for Simplifying a Circuit (Calculation of Equivalent Resistance)

- Remove resistances that are in series with open circuit or in parallel with short circuit.
- Calculate the equivalent resistance of each branch.
- Conclude the overall circuit's equivalent resistance.
- Use of Ohm's Law to find current or voltage of the generator supplying the circuit.

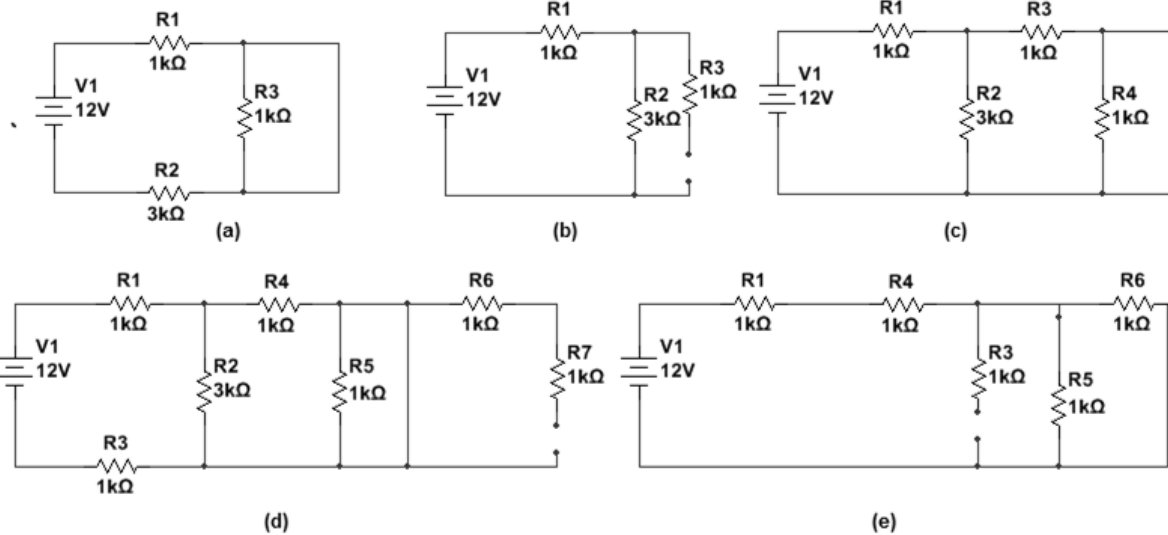
Exercise 1 Calculate the equivalent resistance




Exercise 2 Calculate I

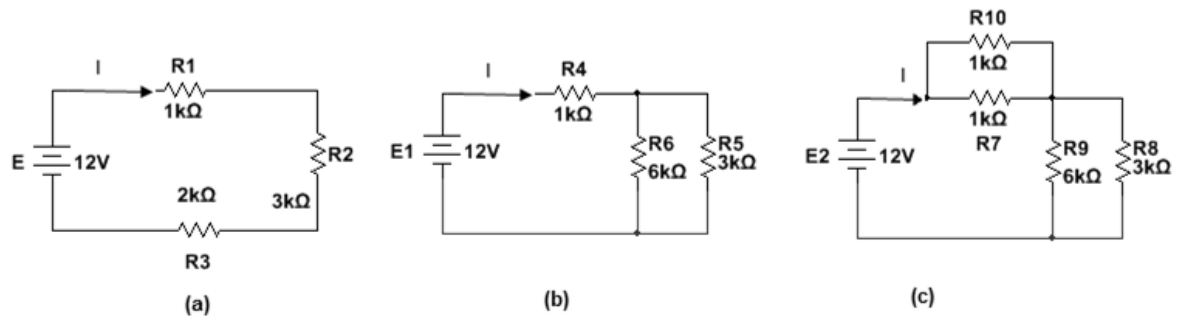

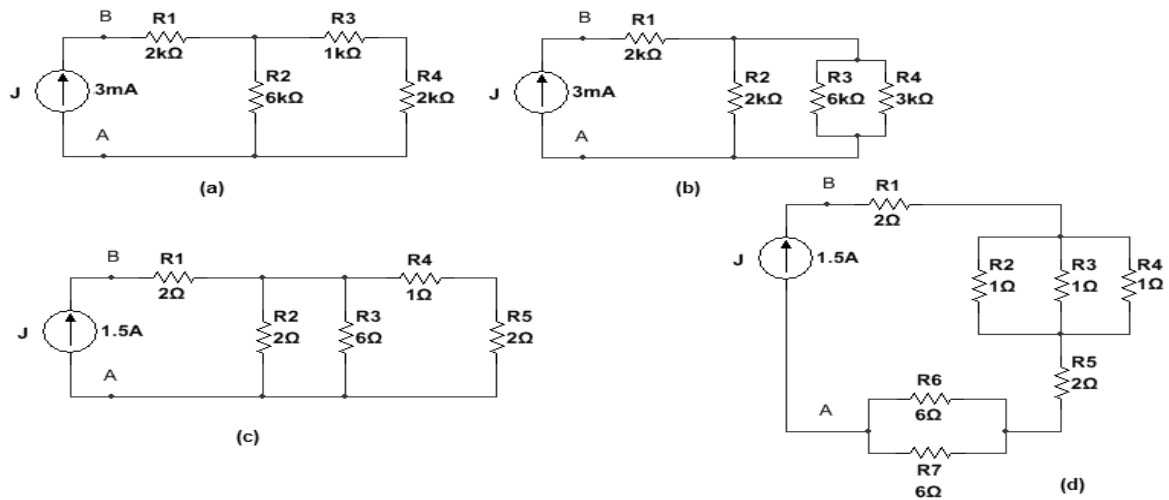Exercise 3 Calculate the electrical voltage between the two points A and B in each of the circuits




Exercise 4 Simplify the electrical circuits and then calculate their respective equivalent resistance

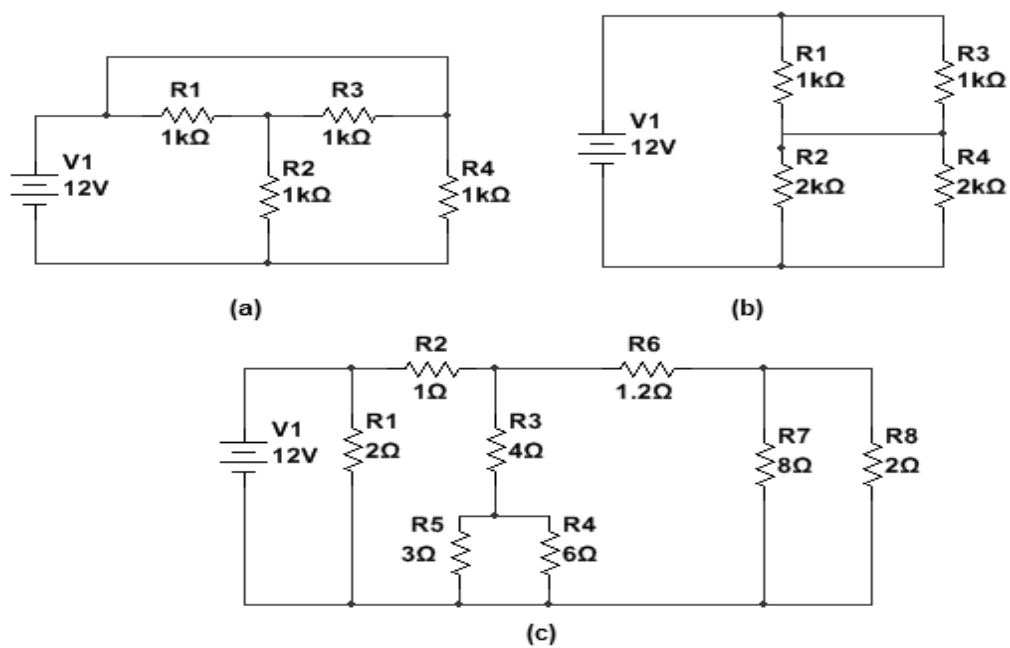

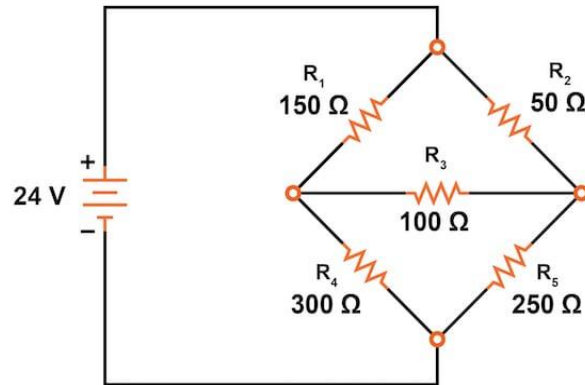Problem 2

Consider the following electrical circuit:




1. Simplify the circuit:
 - Use series and parallel resistor combinations wherever possible.
 - Apply Kennelly's theorem to simplify any delta or star configurations.
 - Redraw the simplified circuit diagram.
2. Calculate the total equivalent resistance of the circuit.
3. Determine the total current flowing through the circuit.
4. Calculate the voltage drop across each resistor.
5. Calculate the power dissipated by each resistor.
6. Verify the power balance principle by showing that the total power supplied by the voltage source equals the sum of the power dissipated by all resistors.
7. If a resistor (e.g., R_3) fails open circuit, how will it affect the current flowing through the other resistors? Explain your reasoning.
8. If a resistor (e.g., R_2) fails short circuit, how will it affect the voltage across the other resistors? Explain your reasoning.

Tutorial 3

Course Notes Kirchhoff's Law

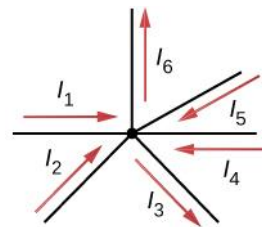I) Kirchhoff's Current Law KCL (Junction Rule or Node rule):

Currents entering a junction in a circuit is equal to currents leaving that junction.



$$\sum I_{\text{in}} = \sum I_{\text{out}}$$

$$I_1 + I_2 + I_4 + I_5 = I_3 + I_6$$

II) Kirchhoff's Voltage Law KVL (Loop Rule or Mesh rule):


The summation of voltages around a mesh or loop is equal to 0.

$$\sum V = 0.$$

	$V - V_1 - V_2 - V_3 = 0$ $V - R_1 \cdot I - R_2 \cdot I - R_3 \cdot I = 0$ $I = V / (R_1 + R_2 + R_3)$ $I = 12 / (1 + 2 + 3)$ $I = 2 \text{ A.}$
--	---

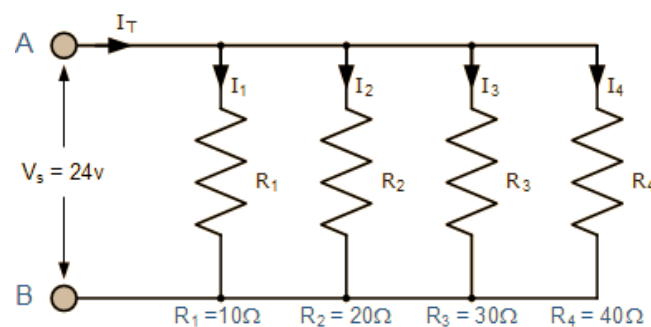Example 1 : (KCL)

For a network of resistors connected in parallel, find all the currents in the circuits.



$$I_1 = \frac{V_s}{R_1} = \frac{24V}{10\Omega} = 2.4\text{amps} \quad I_3 = \frac{V_s}{R_3} = \frac{24V}{30\Omega} = 0.8\text{amps} \quad I_T = I_1 + I_2 + I_3 + I_4$$

$$I_2 = \frac{V_s}{R_2} = \frac{24V}{20\Omega} = 1.2\text{amps} \quad I_4 = \frac{V_s}{R_4} = \frac{24V}{40\Omega} = 0.6\text{amps} \quad I_T = 2.4 + 1.2 + 0.8 + 0.6$$

$$I_T = 5.0\text{Amps}$$


I_T can also be calculated by :

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_T} = \frac{1}{10} + \frac{1}{20} + \frac{1}{30} + \frac{1}{40}$$

$$\frac{1}{R_T} = 0.1 + 0.05 + 0.033 + 0.025$$

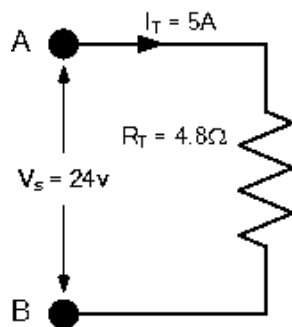
$$\therefore R_T = \frac{1}{0.2083} = 4.8\Omega$$




$$I_T = \frac{V_s}{R_T} = \frac{24}{4.8} = 5\text{Amps}$$

Example 2

Find all currents in this circuit.

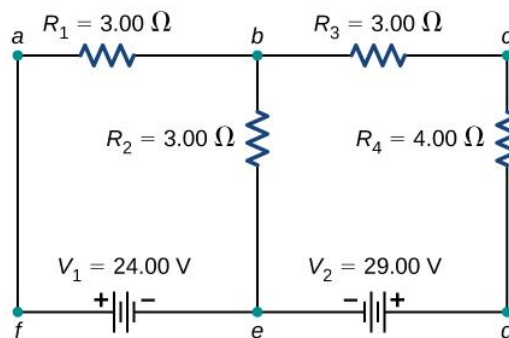

Solution

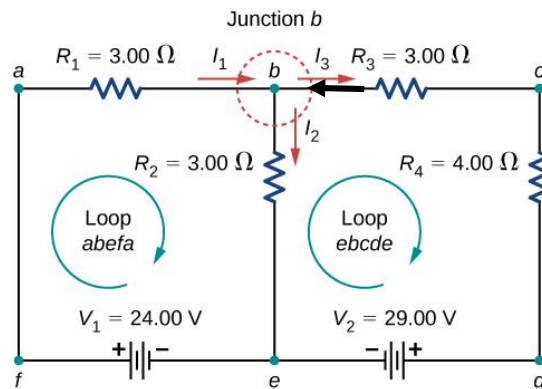

Junction **b** : $I_2 = I_1 + I_3$

$I_1 = ?$ $I_2 = ?$ $I_3 = ?$

Mesh or Loop abefa : $-I_1 R_1 - I_2 R_2 + V_1 = 0$, so $V_1 = I_1 R_1 + I_2 R_2$.

Loop ebcde : $I_2 R_2 + I_3 (R_3 + R_4) - V_2 = 0$, so $V_2 = I_2 R_2 + I_3 (R_3 + R_4)$.

$$\begin{cases} V_1 = I_1 R_1 + I_2 R_2. & \text{eq1} \\ V_2 = I_2 R_2 + I_3 (R_3 + R_4). & \text{eq2} \end{cases}$$

Node b: $I_2 = I_1 + I_3$, we replace in eq1 to obtain: $V_1 = I_1 R_1 + (I_1 + I_3) R_2 = (R_1 + R_2) I_1 + R_2 I_3$ so: $6I_1 + 3I_3 = 24$	Now, eq1 – eq2 to obtain: $V_1 - V_2 = I_1 R_1 - I_3 (R_3 + R_4)$, so: $3I_1 - 7I_3 = -5$
---	--

$$\begin{cases} 6I_1 + 3I_3 = 24 & \text{eq1} \\ 3I_1 - 7I_3 = -5 & \text{eq2} \end{cases}$$

$$\text{Eq1} - 2 \times (\text{eq2}) : 6I_1 + 3I_3 - 6I_1 + 14I_3 = 24 + 10$$


$$17I_3 = 34, \mathbf{I_3 = 2A}$$

$$\text{Eq1} : 6I_1 + 6 = 24, \mathbf{I_1 = 3A}$$

$$\text{Finally: } I_2 = I_1 + I_3 = 2 + 3, \mathbf{I_2 = 5A}$$


Homework's Assignment

Find the currents flowing in the circuit

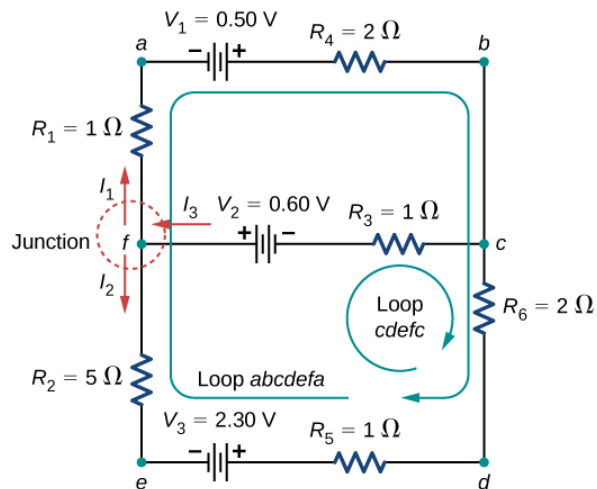

Final Solution: $I_1=0,2A$ $I_2=0,3A$ $I_3=0,5A$

Problem 3

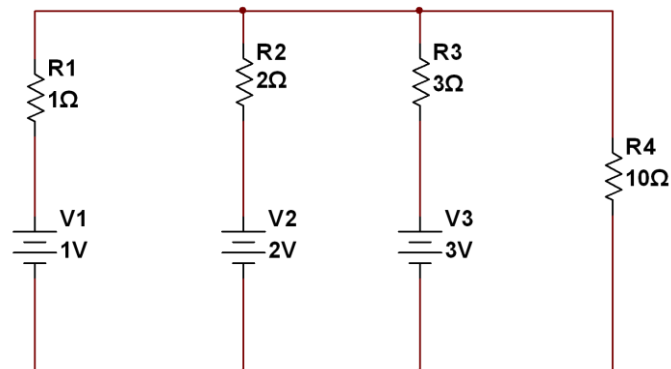

1. **Apply Kirchhoff's Current Law (KCL)** at all the nodes in the circuit. Write down the KCL equations for each node.
2. **Apply Kirchhoff's Voltage Law (KVL)** to all the independent loops in the circuit. Write down the KVL equations for each loop.
3. **Using the KCL and KVL equations obtained in steps 1 and 2, set up a system of linear equations.**
4. **Solve the system of linear equations** to determine the current flowing through each resistor.
5. **Verify the power balance principle:**
 - Calculate the power supplied by each voltage source.
 - Calculate the power dissipated by each resistor.
 - Show that the sum of the powers supplied equals the sum of the powers dissipated.


Tutorial 4

Course Notes Voltage & Current divider

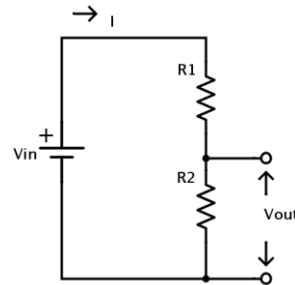I) Voltage Divider


Voltage divider is a configuration of resistors connected in series that divides a voltage into smaller voltages. The voltage in each resistor is found by its resistance over the total resistance of the circuit.

$$V_{out} = \frac{R_2}{R_1 + R_2} V_{in}$$



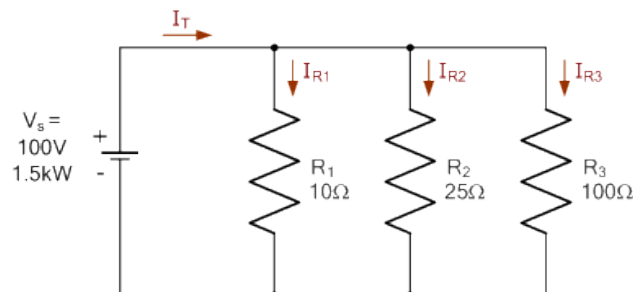
II) Current Divider

Current divider circuits have multiple parallel branches that allow current to flow through different paths, while maintaining the same voltage across all parallel components.




$P = V_s \times I_T$ $I_T = \frac{P}{V} = \frac{1500}{100} = 15 \text{ Amps}$	$R_{EQ} = \left[\frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} \right]$ $R_{EQ} = \left[\frac{1}{\frac{1}{10} + \frac{1}{25} + \frac{1}{100}} \right]$ $R_{EQ} = \frac{1}{0.15} = 6.667 \Omega$	$I_{R1} = I_T \left(\frac{R_{EQ}}{R_1} \right) = 15 \left(\frac{6.667}{10} \right) = 10 \text{ Amps}$ $I_{R2} = I_T \left(\frac{R_{EQ}}{R_2} \right) = 15 \left(\frac{6.667}{25} \right) = 4 \text{ Amps}$ $I_{R3} = I_T \left(\frac{R_{EQ}}{R_3} \right) = 15 \left(\frac{6.667}{100} \right) = 1 \text{ Amps}$
---	--	--

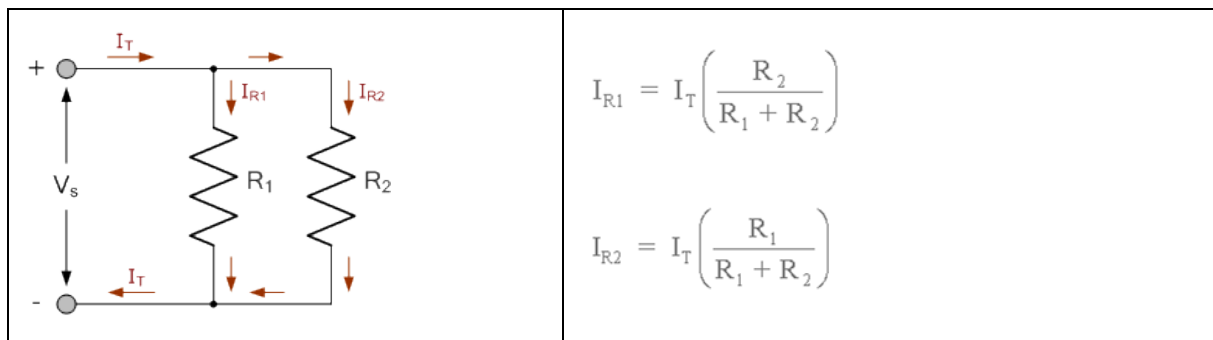Example of the case of 2 parallel resistors:









HomeWork's Assignment:

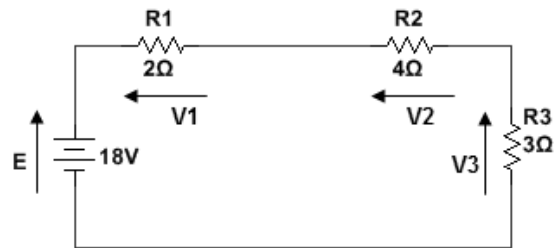
Exercise 1 Calculate voltages across each resistors using voltage divider rule



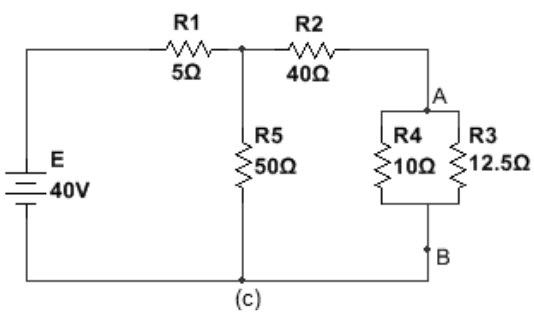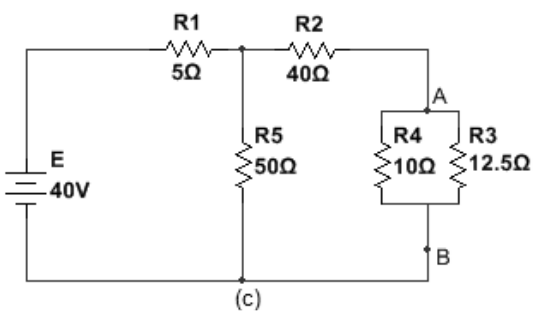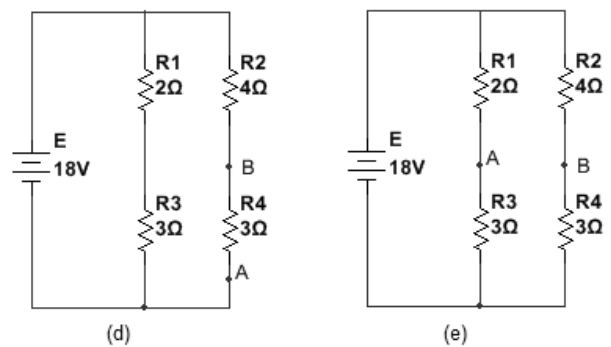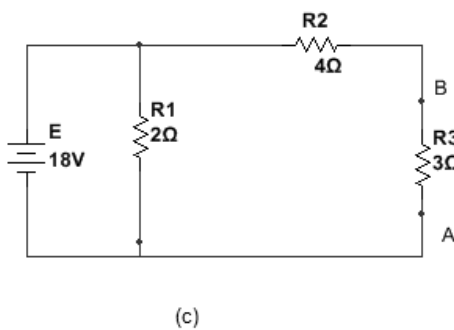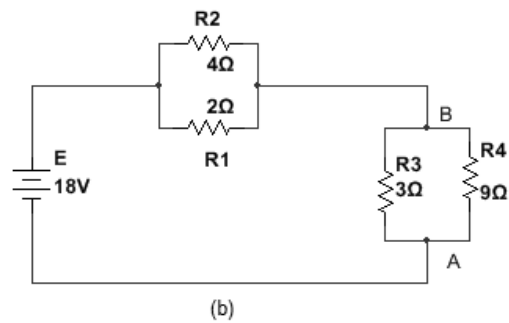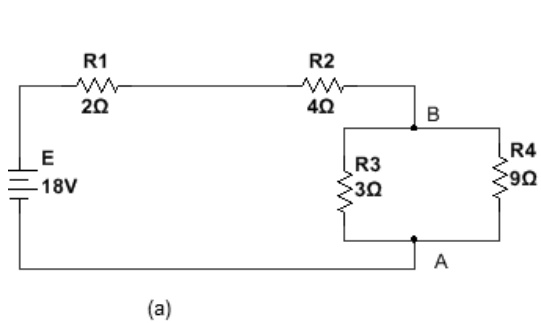
Exercise 2 Calculate the voltage between A & B using voltage divider rule



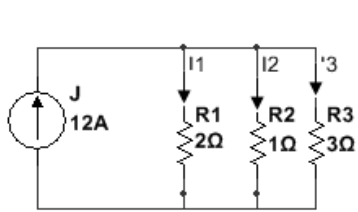
Exercise 3 Using Current divider rule, calculate currents I_1 , I_2 , I_3 & I_4




(a)

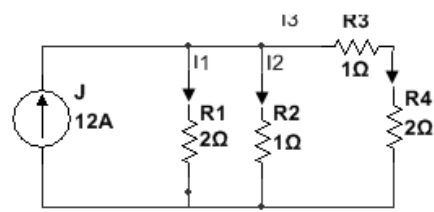


(b)

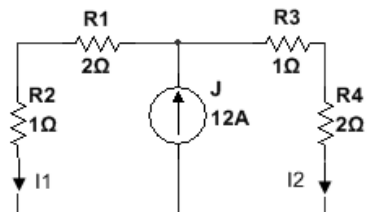

(c)

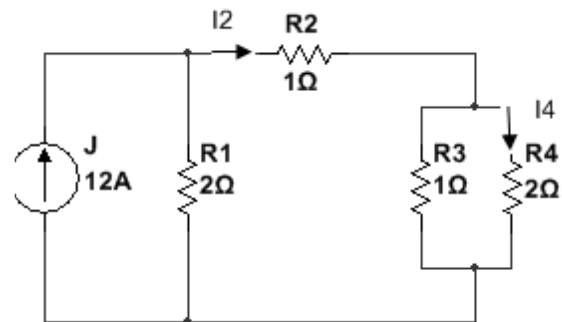

Problem 4

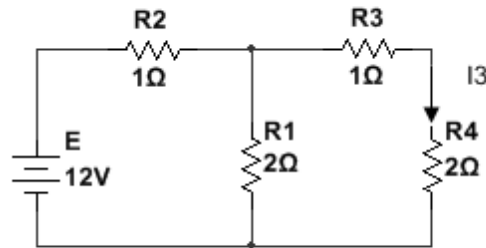


1. Calculate the total resistance (R_{eq}) of the series circuit.
2. Using the Voltage Divider Rule, calculate the voltage drop across each resistor (V_3 , V_4) & (V_1 , V_2).
3. Calculate the total current (I) flowing through the circuit.
4. Now, assume that a fourth resistor ($R_5 = 1\Omega$) is connected in parallel with R_4 .
 - Calculate the equivalent resistance of the parallel combination of R_3 , R_4 and R_5 .
 - Calculate the new total resistance of the circuit.
 - Calculate the new total current (I') flowing through the circuit.
5. Using the Current Divider Rule, calculate the current flowing through R_4 and R_5 in the modified circuit.

Tutorial 5

Course Notes Superposition theorem

Superposition Theorem states that any the total response (current or voltage) at a point in a circuit can be found by the calculation of the sum of the responses caused by each source acting individually while the others are considered inactive [3]

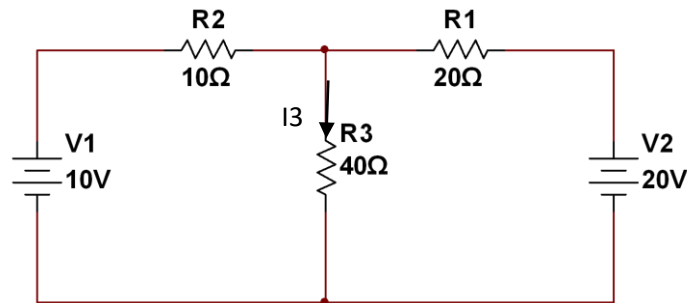Example: find current I_3 flowing via R_3 using superposition theorem



Superposition theorem:

$$I_{R3} = I_{R3(1)} + I_{R3(2)}$$


$I_{R3(1)}$: the current flowing through R_3 as a result of V_1 acting alone in the circuit

$I_{R3(2)}$: the current flowing through R_3 as a result of V_2 acting alone in the circuit

Solution

Current $I_{R3(1)}$

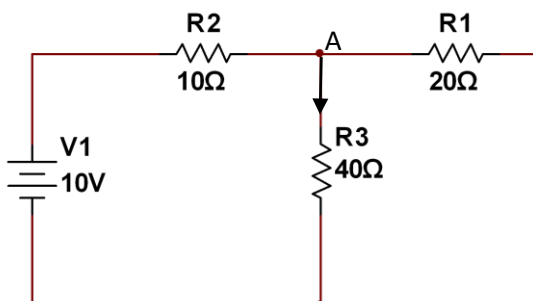First, we change V_2 by short-circuit so that V_1 will acting alone on the circuit



20Ω Resistor in Parallel with the 40Ω Resistor

$$R_{EQ1} = \frac{R_2 \times R_3}{R_2 + R_3} = \frac{20 \times 40}{20 + 40} = 13.33\Omega$$

Using voltage divider, we calculate V_A at the node A

$$V_A = V_1 \left(\frac{R_{EQ1}}{R_1 + R_{EQ1}} \right) = 10 \left(\frac{13.33}{10 + 13.33} \right) = 5.71 \text{ volts}$$

Then ,


$$I_{R3(1)} = V_A / R_3 = 5.71 / 40 = 0.143 \text{ A} = 143 \text{ mA}$$

So, the current flowing through R_3 as a result of V_1 acting alone in the circuit is **143mA**.

Current $I_{R3(2)}$

We Use the same method as before to calculate the current flowing through R_3 being driven by only voltage V_2 .

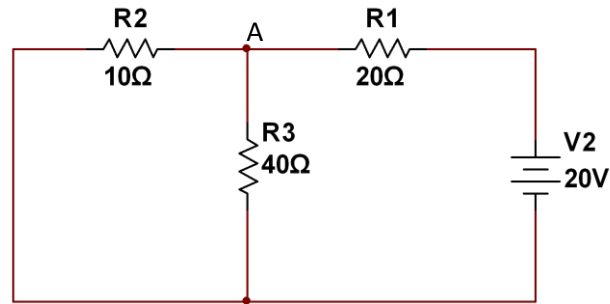V_1 is replaced by a short circuit. V_2 is acting alone in the circuit.



10Ω Resistor in Parallel with the 40Ω Resistor

$$R_{EQ2} = \frac{R_1 \times R_3}{R_1 + R_3} = \frac{10 \times 40}{10 + 40} = 8\Omega$$

Using voltage divider, we find voltage at node A as a result of V_2 .

$$V_A = V_2 \left(\frac{R_{EQ2}}{R_2 + R_{EQ2}} \right) = 20 \left(\frac{8}{20 + 8} \right) = 5.71 \text{ volts}$$

Then,


$$I_{R3(2)} = V_A / R_3 = 5.71 / 40 = 0.143 \text{ A} = 143 \text{ mA}$$

So, the current flowing through R_3 as a result of V_2 acting alone in the circuit is **143mA**.


Now to find the final value and direction of I_{R3} we calculate the sum of $I_{R3(1)}$ and $I_{R3(2)}$:

$$I_{R3} = I_{R3(1)} + I_{R3(2)} = 0.143 + 0.143 = 0.286 = \mathbf{286mA}$$

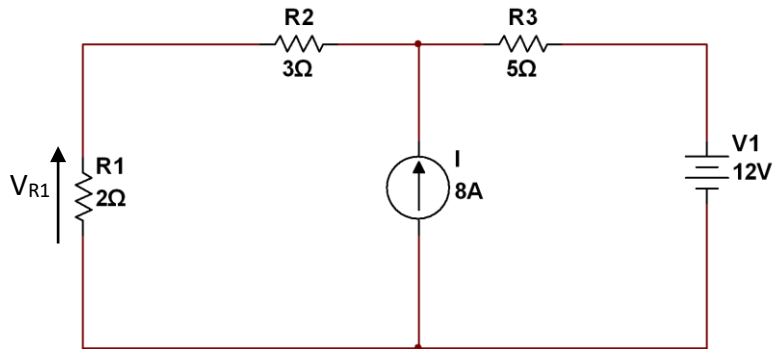Example2: Using superposition theorem, find V_{R1}



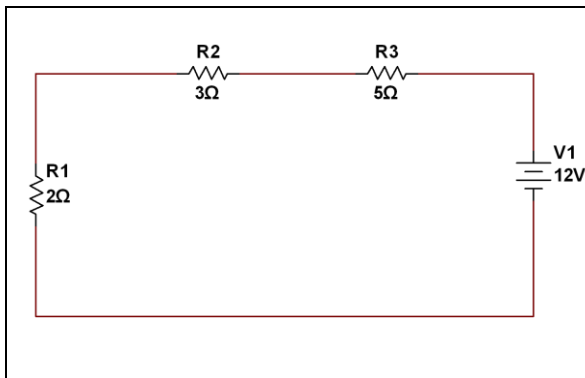
Superposition theorem: $V_{R1} = V_{R1(1)} + V_{R1(2)}$



$$I_1 = V_1 / (R_1 + R_2 + R_3) = 20 / 10 = 2 \text{ A}$$

The individual voltage drop across resistor R_1 is calculated as being:
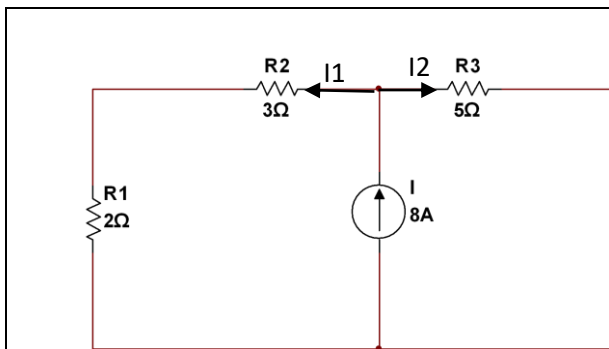
$$V_{R1(1)} = I_1 \times R_1 = 2 \times 2 = \mathbf{4 \text{ volts}}$$



$$I_1 = (R_3 / (R_3 + R_1 + R_2)) \times I$$

$$= 4 \text{ A}$$





Voltage across R_1 :

$$V_{R1(2)} = I_1 \times R_1 = 4 \times 2 = \mathbf{8 \text{ volts}}$$

$$\text{Finally, } V_{R1} = V_{R1(1)} + V_{R1(2)} = 4\text{V} + 8\text{V} = \mathbf{12 \text{ Volts}}$$








Exercises (Homework's Assignment)

Exercise 1 Calculate I using superposition theorem in each of the following circuits.

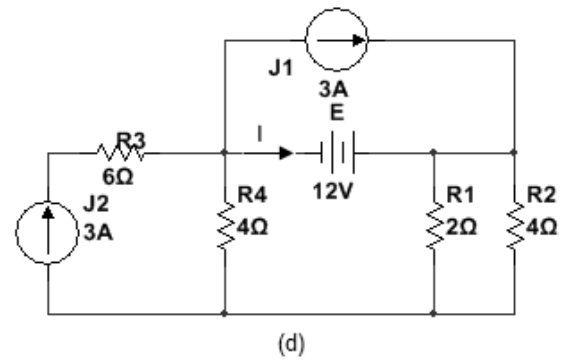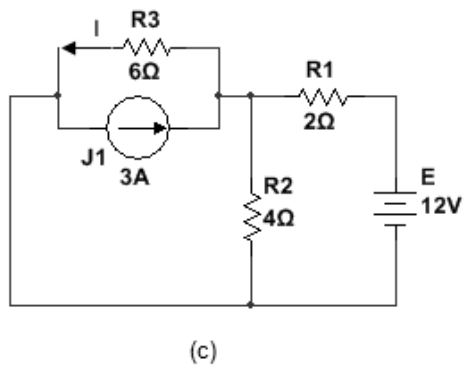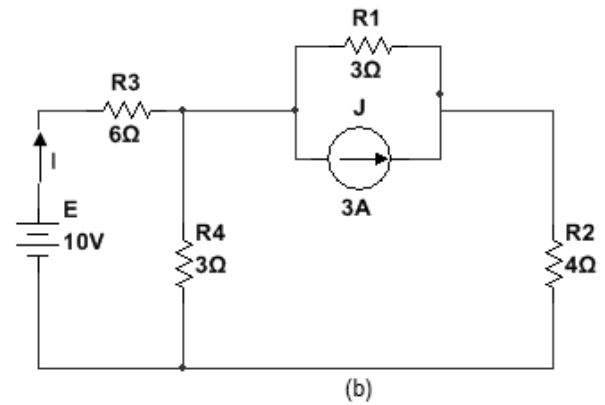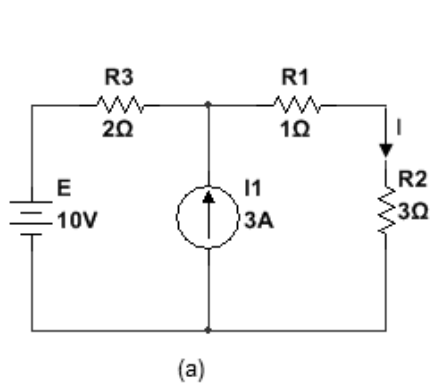

Problem 5

Calculate voltage between points A & B using superposition theorem in each of the following circuits

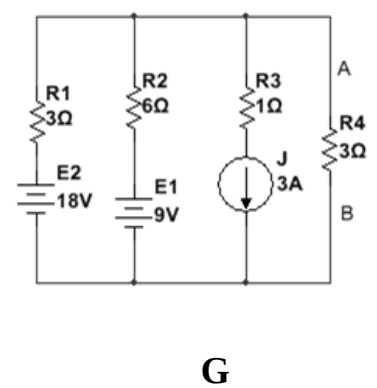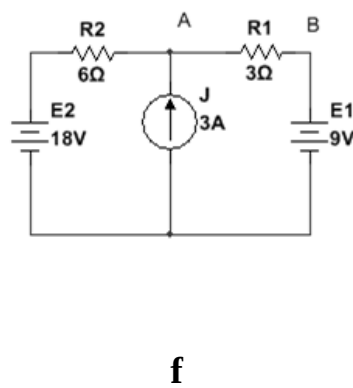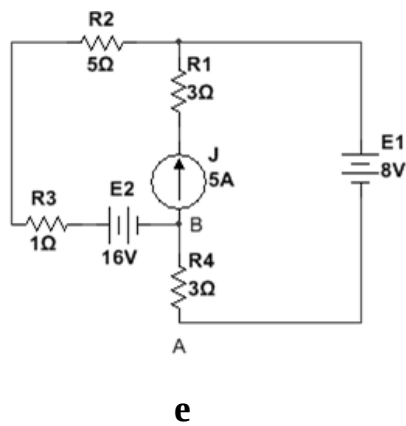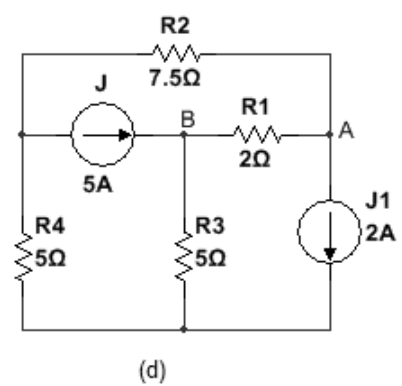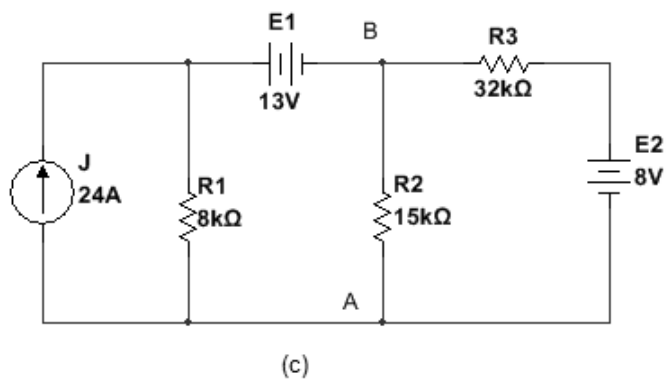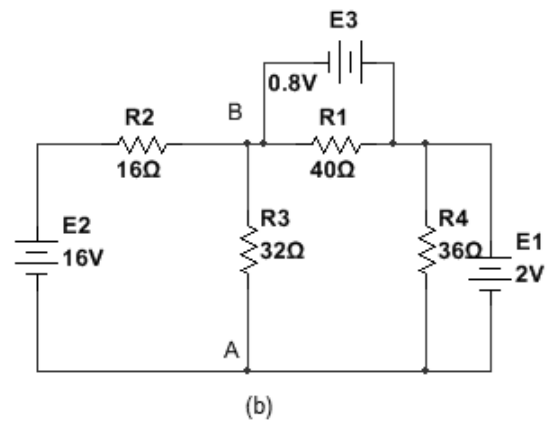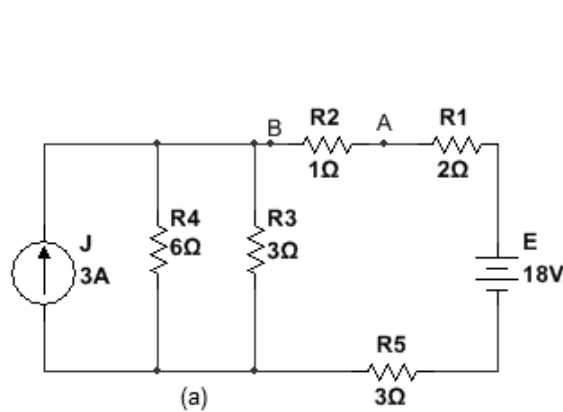


Tutorial 6

Course Notes Thevenin theorem

Thevenin Theorem states that a complex circuit can be simplified into a circuit with a single voltage source and a single resistor connected in series. This equivalent circuit will produce the same voltage and current at its terminals as the original circuit [1].

Example

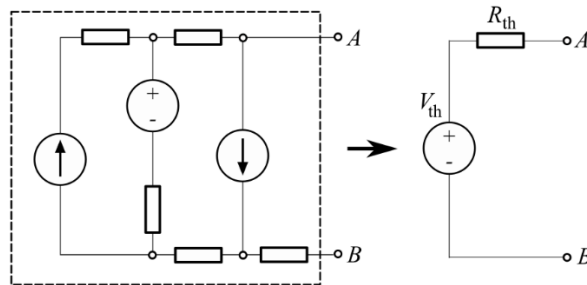


A complex network of resistors and voltage sources can be simplified into only one resistor (R_{th}) and one voltage source (V_{th}), with :

- R_{th} is the equivalent resistance between A and B.
- V_{th} is the voltage measured between A and B when there's no load connected.

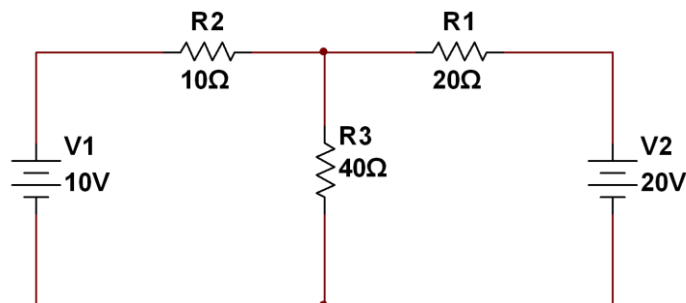Example


Find current flowing through the 40 ohm resistor using thevenin theorem.



Solution

- First, we start by excluding the middle load resistor between points A and B, and eliminate the power supply sources.

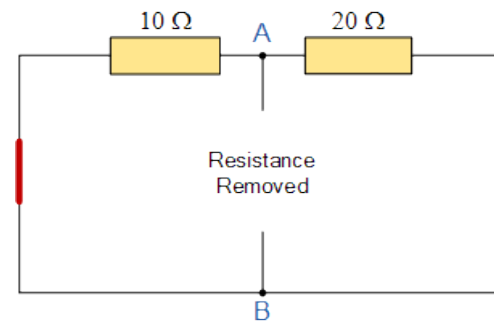- Then, Calculate the equivalent resistance R_{th} between A and B.




To find the thevenin resistor R_{th} :

10Ω Resistor in Parallel with the 20Ω Resistor

$$R_T = \frac{R_1 \times R_2}{R_1 + R_2} = \frac{20 \times 10}{20 + 10} = 6.67\Omega$$

- The voltage V_{th} is calculated by measuring the voltage between terminals A and B when the load resistor R_L is disconnected.

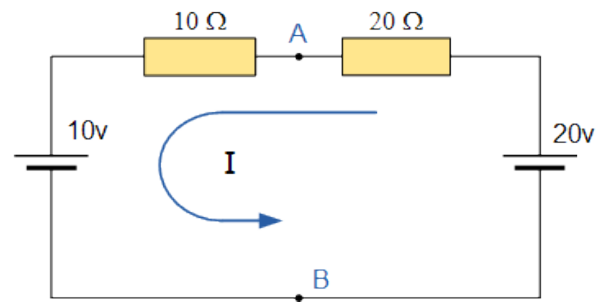
$$I = \frac{V}{R} = \frac{20v - 10v}{20\Omega + 10\Omega} = 0.33 \text{ amps}$$



Mesh law :

$$V_{th} = V_{AB} = V_2 - R_1 \times I = 20 - 20 \times 0.33 = 13.33 \text{ volts.}$$

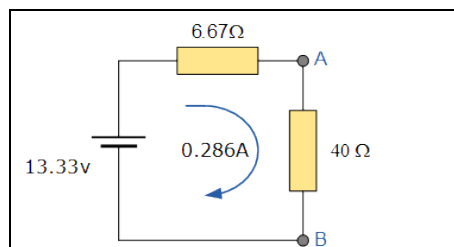
The Thevenin equivalent circuit comprises a 6.67 ohms resistor connected in series with a 13.33-volt voltage source. If we reattach the 40-ohm resistor to this equivalent circuit, we have:




$$I = \frac{V}{R} = \frac{13.33v}{6.67\Omega + 40\Omega} = 0.286 \text{ amps}$$

Exercises Homework's Assignment

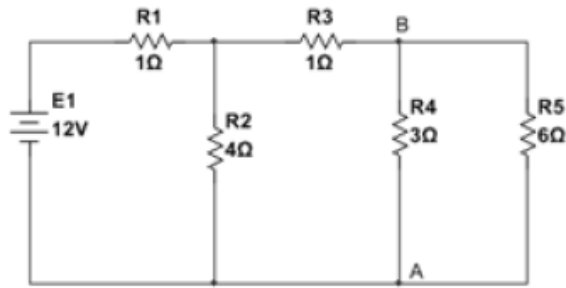
Exercise 1 Calculate voltage across R_4 using Thevenin theorem in each of the following circuits.




(a)

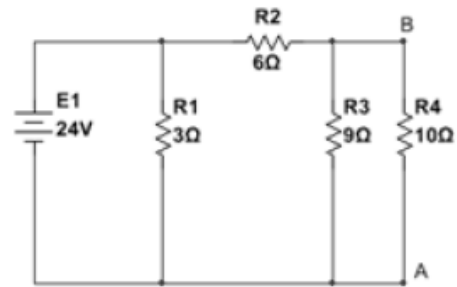

(b)

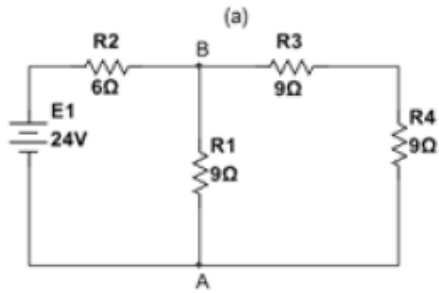


(c)

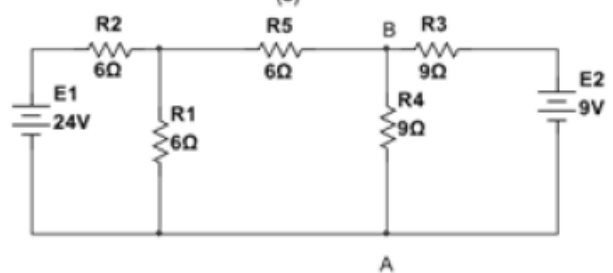

(d)

Problem 6

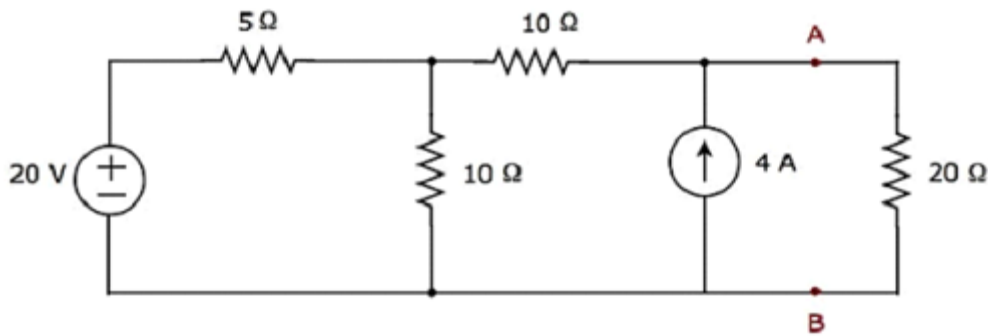

Find the Thevenin equivalent voltage (V_{th}) across terminals A and B.

- Remove the load resistor (R_L) from the circuit.
- Calculate the open-circuit voltage between terminals A and B using appropriate circuit analysis techniques (e.g., nodal analysis, mesh analysis).

Find the Thevenin equivalent resistance (R_{th}) across terminals A and B.

- Replace all voltage sources with short circuits.
- Replace all current sources with open circuits.
- Calculate the equivalent resistance between terminals A and B.

Draw the Thevenin equivalent circuit.

- Represent the original circuit with a single voltage source (V_{th}) in series with a single resistor (R_{th}).

Reconnect the load resistor (R_L) to the Thevenin equivalent circuit.

- Calculate the current flowing through the load resistor (R_L) using Ohm's Law.

Compare the current through R_L calculated in step 4 with the current through R_L in the original circuit.


- Verify that both methods yield the same result.

Tutorial 7

Course Notes: Norton theorem

Norton's Theorem is a method for simplifying complex circuits.

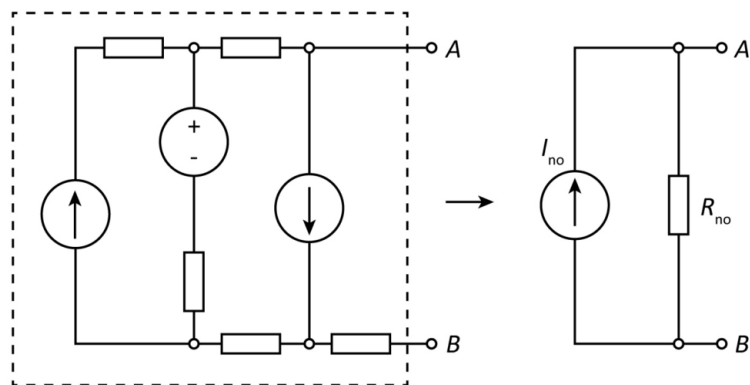A circuit with multiple sources will be replaced by only one current source and one parallel resistor [2].




I_{no} : current flowing between terminals A and B if they are shorted.

R_N the Norton resistance is the resistance measured looking into the circuit from its terminals A and B (similar to Thevenin).

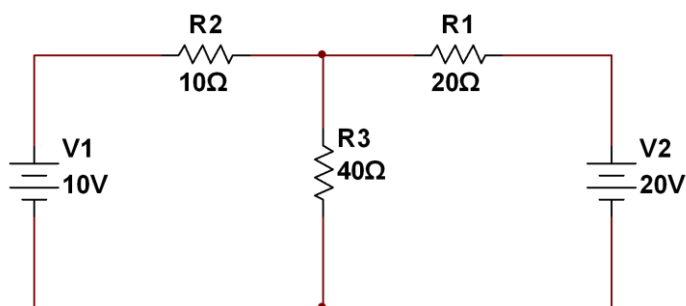Example

Calculate current flowing through the 40 ohm resistor using thevenin theorem.




Calculation of I_N

Remove the 40 ohm load resistor and connect terminals A and B directly together.

$$I_1 = \frac{10\text{V}}{10\Omega} = 1\text{amp}, \quad I_2 = \frac{20\text{V}}{20\Omega} = 1\text{amp}$$

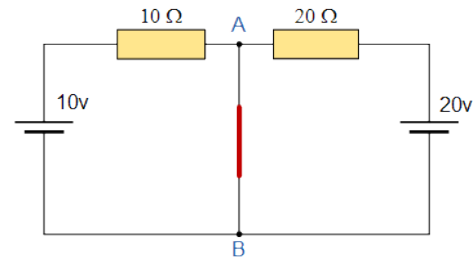therefore, $I_{\text{short-circuit}} = I_1 + I_2 = 2\text{amps}$




Calculation of R_N

Short circuit the power sources & remove the 40 ohm resistor to open-circuit terminals A and B

10Ω Resistor in Parallel with the 20Ω Resistor
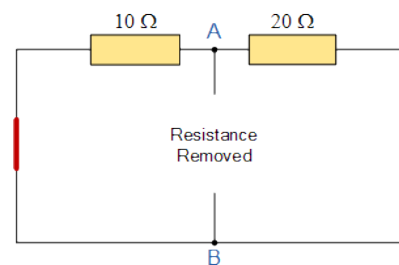
$$R_T = \frac{R_1 \times R_2}{R_1 + R_2} = \frac{20 \times 10}{20 + 10} = 6.67\Omega$$



Norton Theorem Equivalent Circuit :


$R_T = \frac{R_1 \times R_2}{R_1 + R_2} = \frac{6.67 \times 40}{6.67 + 40} = 5.72\Omega$	$V_{A-B} = I \times R = 2 \times 5.72 = 11.44\text{V}$

So,


$$I = \frac{V}{R} = \frac{11.44}{40} = 0.286\text{ amps}$$

Exercises (Homework's Assignment)

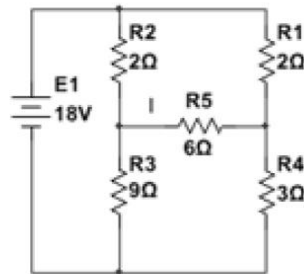
- 1) Calculate current I using Norton equivalent circuit in each of the following circuits




(b)

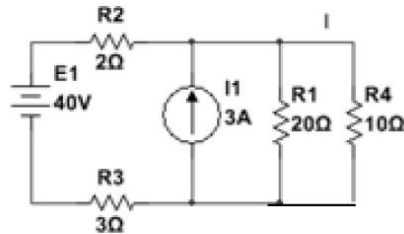

(c)

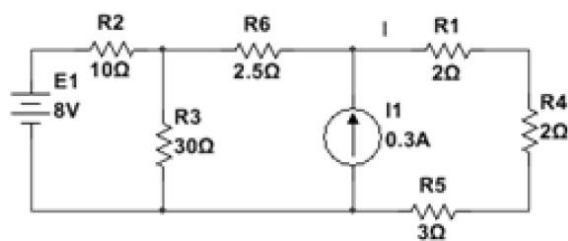


(d)

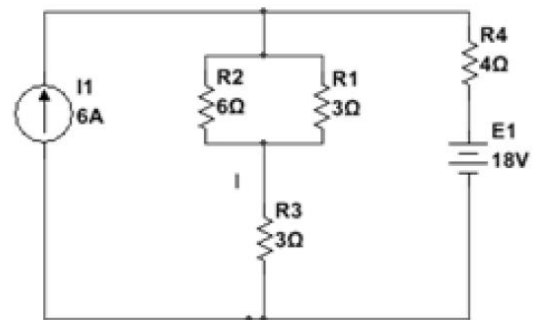

(e)

Problem 7

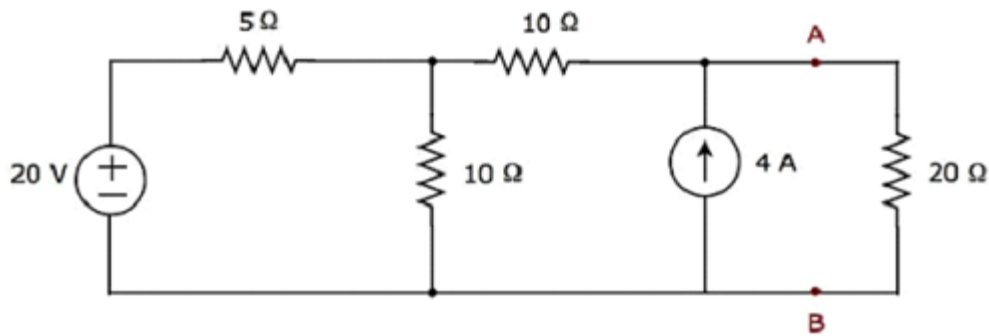

1. **Find the Norton equivalent current (I_N) across terminals A and B.**
 - Remove the load resistor (R_L) from the circuit.
 - Calculate the short-circuit current flowing between terminals A and B.
2. **Find the Norton equivalent resistance (R_N) across terminals A and B.**
 - Replace all voltage sources with short circuits and current sources with open circuits.
 - Calculate the equivalent resistance between terminals A and B.
3. **Draw the Norton equivalent circuit.**
 - Represent the original circuit with a single current source (I_N) in parallel with a single resistor (R_N).
4. **Reconnect the load resistor (R_L) to the Norton equivalent circuit.**
 - Calculate the current flowing through the load resistor (R_L) using current divider rule.
5. **Compare the current through R_L calculated in step 4 with the current through R_L in the original circuit.**
 - Verify that both methods yield the same result.

Tutorial 8

Course Notes: Millman Theorem

Millman's Theorem states that in a circuit with many parallel branches containing voltage sources, the equivalent voltage across the terminals is the sum of each branch's voltage divided by the sum of the reciprocals of the branch impedances [3].

This method can only be used for circuits that can be rearranged into this parallel branch structure.


Equivalent Voltage (V_{eq}):

$$V_{eq} = (\sum (V_i / R_i)) / (\sum (1 / R_i))$$

where:


- V_i is the voltage of the i th branch
- R_i is the resistance of the i th branch

Example

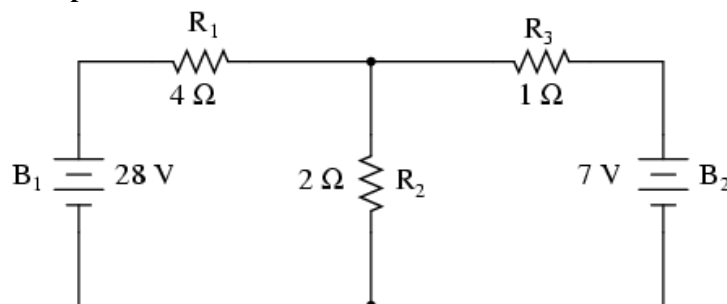


Solution

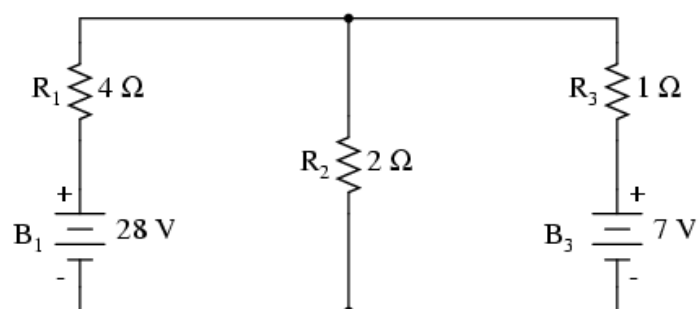
Let's redraw the circuit in a way that shows the parallel branches more clearly.



Millman's Theorem Equation	
$\frac{\frac{E_{B1}}{R_1} + \frac{E_{B2}}{R_2} + \frac{E_{B3}}{R_3}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = \text{Voltage across all branches}$	$\frac{\frac{28 \text{ V}}{4 \Omega} + \frac{0 \text{ V}}{2 \Omega} + \frac{7 \text{ V}}{1 \Omega}}{\frac{1}{4 \Omega} + \frac{1}{2 \Omega} + \frac{1}{1 \Omega}} = 8 \text{ V}$

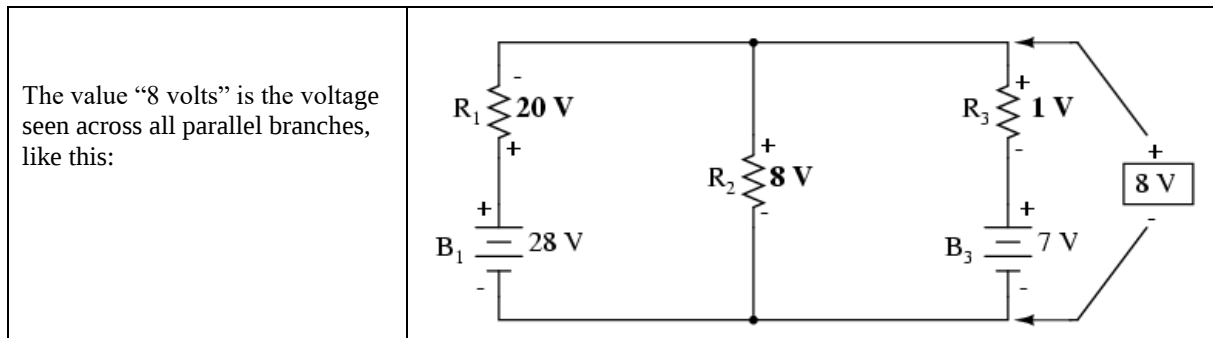


Example 2

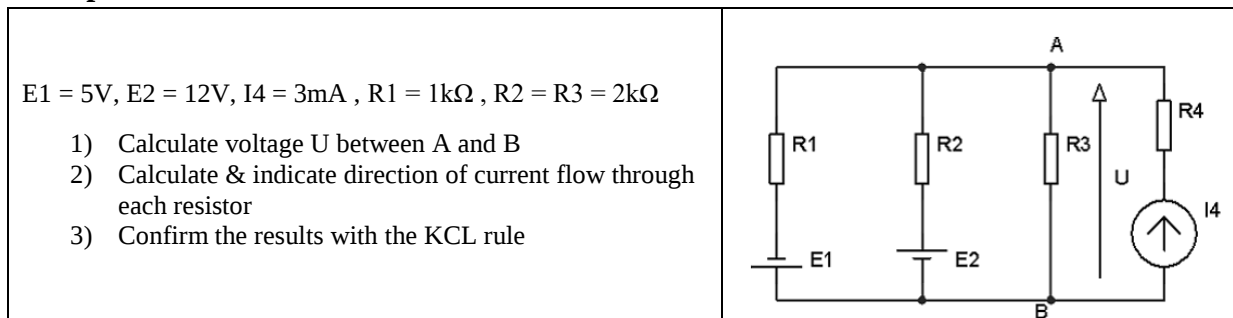

Solution

$$1) \quad U = \frac{\frac{-E_1}{R_1} + \frac{E_2}{R_2} + I_4}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = \frac{\frac{-5}{1} + \frac{12}{2} + 3}{\frac{1}{1} + \frac{1}{2} + \frac{1}{2}} = -2\text{V}$$

2)

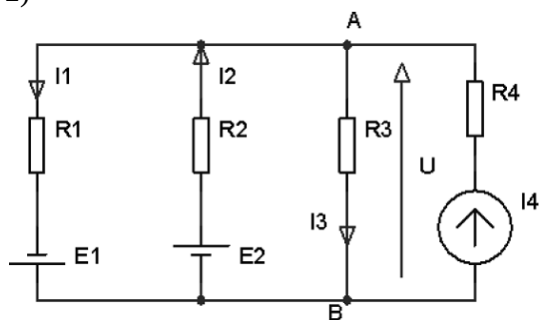

$$U + E_1 = R_1 I_1 \rightarrow I_1 = (2\text{V} + 5\text{V}) / 1\text{k}\Omega \rightarrow I_1 = 7\text{mA}$$


$$U - E_2 = -R_2 I_2 \rightarrow I_2 = -(2\text{V} - 12\text{V}) / 2\text{k}\Omega \rightarrow I_2 = 5\text{mA}$$

$$U = R_3 I_3 \rightarrow I_3 = 2\text{V} / 2\text{k}\Omega \rightarrow I_3 = 1\text{mA}$$

$$3) \quad I_1 - I_2 + I_3 - I_4 = 7 - 5 + 1 - 3 = 0$$

Exercises: (Homework Assignment)

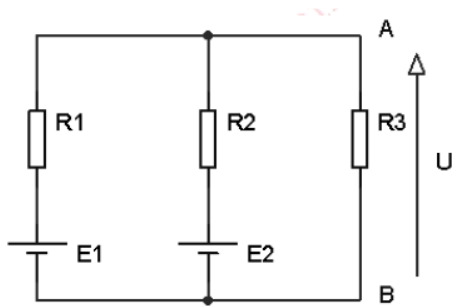Exercise1: Calculate U using Millman's theorem.




$$E_1 = 5\text{volts}$$

$$E_2 = 12\text{ volts}$$


$$R_1 = 1\text{ kOhms}$$

$$R_2 = R_3 = 2\text{ kOhms}$$

Exercise 2 Find the current I using Millman's theorem.

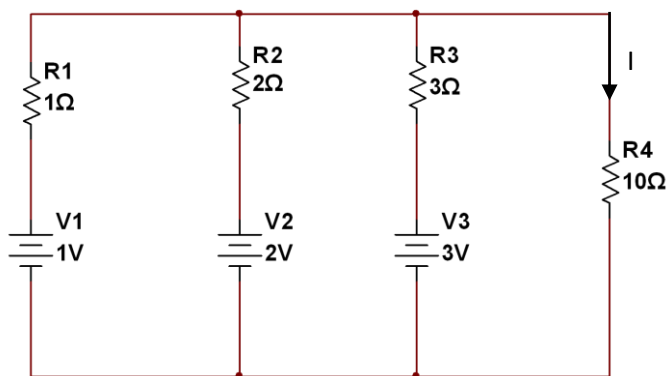

Problem 8

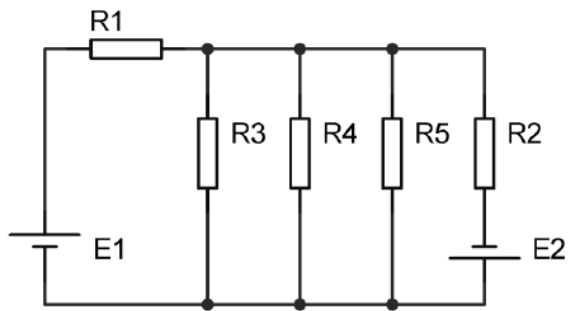

$E1=10V$ $E2=5V$ $R1=R2=1k$ $R3=R4=R5=1,5k$

- 1) **Apply Millman's Theorem** to determine the equivalent voltage (V_m) across the parallel branches.
- 2) Calculate and indicate the direction of the current flowing through each resistor
- 3) Verify the KCL node rule.

Acronym List

DC = Direct Current

AC = Alternating Current

I = current

V : Voltage ("U" is also used for voltage)

R : Resistance

E :Energy

P : Power

A = Ampere

v : volts

Ω : Ohm

Bibliography

Here are some references on electrical circuits or basics of electricity with exercises and solutions

[1] Dorf, Richard C., and James A. Svoboda. ***Introduction to Electric Circuits***. Hoboken, NJ: Wiley, 2015. ISBN: 978-1119560983.

[2] Seymour, Charles D., and Herman W. Cooke. ***Basic Electricity***. Mineola, NY: Dover Publications, 2013. ISBN: 978-0486495708.

[3] Johnson, David E., and Johnny R. Johnson. ***Electric Circuit Analysis***. Hoboken, NJ: Wiley, 2016. ISBN: 978-1119235385.

[4] Patrick, Dale R., and Stephen W. Fardo. ***Electricity and Electronics Fundamentals***. Clifton Park, NY: Delmar Cengage Learning, 2012. ISBN: 978-1111128538.