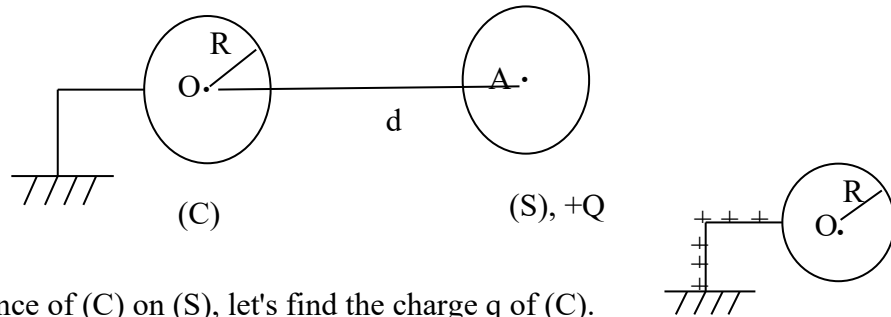




**Correction of SW N° 03**  
**Conductors and capacitors**


**Exercise 1**



Before influence,

Neglecting the influence of (C) on (S), let's find the charge q of (C).

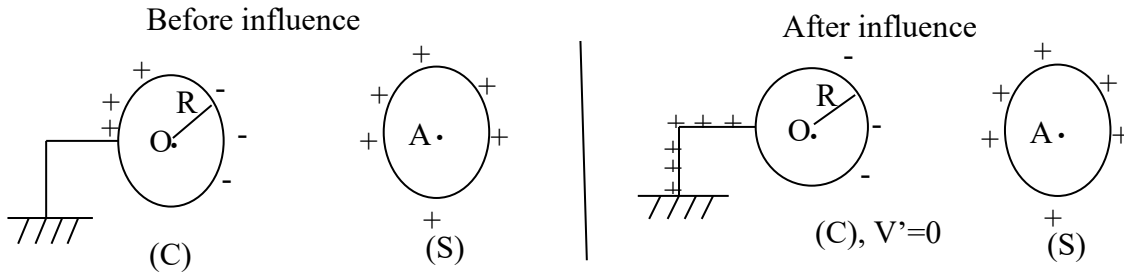Remember that when the conductor is connected to the ground, positive charges flow towards the ground and the potential  $V=0$ .



After the influence, positive charges flow to ground and the conductor (C) will have a negative charge and zero potential.  $V_C' = 0$

$$V_C' = V_C + V_{S/C} = 0$$

with  $V_C$ : is the potential of (C) before influence and  $V_{S/C}$ : is the potential of (C) after influence of (S) on (C).


$$V_C = \frac{kq_C}{R}$$

$$V_{S/C} = \frac{kQ_S}{d} \text{ with } (Q_S = +Q)$$

$$\text{So } V_C' = \frac{kq_C}{R} + \frac{kQ}{d} = 0$$

$$\Rightarrow q_C = -\frac{QR}{d} \text{ with } d = OA$$

**Exercise 2**

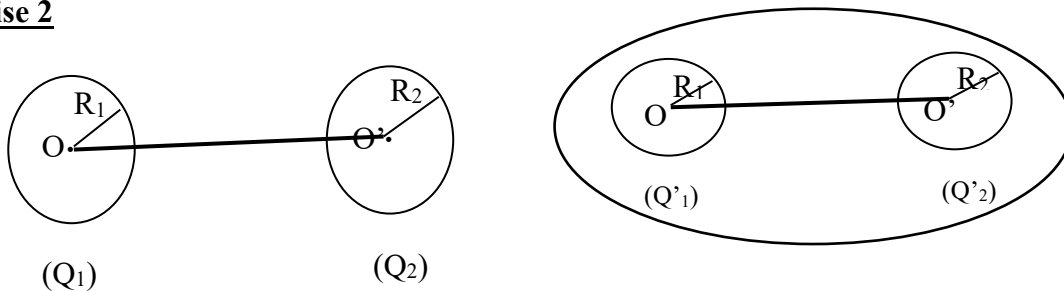

Let's find  $Q1'$  and  $Q2'$  after influence:



By connecting the two conductors with a wire ; a single conductor is created with  $Q_1$  and  $Q_2$  are the charges of the two conductors.

**After influence** when this conductor is in electrostatic equilibrium:

- The potential is constant:  $V_1' = V_2' \Rightarrow \frac{kQ_1'}{R_1} = \frac{kQ_2'}{R_2}$  So  $\frac{Q_1'}{R_1} = \frac{Q_2'}{R_2}$

- The total charge in the formed conductor is the sum of the charges of the two conductors, since the charge carried by the wire is neglected.

$$Q_1' + Q_2' = Q_1 + Q_2$$

$$\begin{cases} \frac{Q_1'}{R_1} = \frac{Q_2'}{R_2} \\ Q_1' + Q_2' = Q_1 + Q_2 \end{cases} \Rightarrow \begin{cases} \frac{Q_1'}{2} = \frac{Q_2'}{3} \\ Q_1' + Q_2' = 25 \end{cases}$$

$$\Rightarrow \begin{cases} Q_1' = 2 \frac{Q_2'}{3} \\ 2 \frac{Q_2'}{3} + Q_2' = 25 \end{cases} \text{ so } Q_2' = 15 \mu\text{C} = Q_2 \text{ et } Q_1' = 10 \mu\text{C} = Q_1$$

The charges on the two conductors have not changed, so there has been no charge displacement, as the two conductors are far apart and the charge on the wire is negligible.

### Exercise 3

1- equivalent capacity

$C_1$  and  $C_2$  in *paralelle*

$$C_{12} = C_1 + C_2 = 1 + 2 = 3 \mu\text{F}$$

$$1/C_{eq} = 1/C_{12} + 1/C_3 + 1/C_4 = 1/3 + 1/3 + 1/3 = 1$$

so  $C_{eq} = 1 \mu\text{F}$

The charge on each capacitor

We have  $Q_{eq} = Q_{12} = Q_3 = Q_4 = C_{eq} \cdot U = 12 \cdot 1 = 12 \mu\text{C}$

so  $Q_3 = Q_4 = 12 \mu\text{C}$

we have also  $C_1$  and  $C_2$  in *paralelle* so  $U_{12} = U_1 = U_2 \Rightarrow Q_{12} / C_{12} = Q_1 / C_1 = Q_2 / C_2$

$$Q_{eq} = Q_{12} = 12 \mu\text{C} \Rightarrow U_{12} = Q_{12} / C_{12} = 12 \cdot 10^{-6} / 3 \cdot 10^{-6} = 4 \text{ V}$$

so  $Q_1 / C_1 = 4 \text{ V} \Rightarrow Q_1 = 4 \cdot C_1 = 4 \mu\text{C}$

In the same way  $Q_2 / C_2 = 4 \Rightarrow Q_2 = 4 \cdot C_2 = 8 \mu\text{C}$

2- Potential difference across each capacitor (direct method)

$$U_1 = U_2 = U_{12} = Q_1 / C_1 = 4 \text{ V} \text{ and } U_3 = Q_3 / C_3 = 4 \text{ V} \text{ then } U_4 = Q_4 / C_4 = 4 \text{ V}$$

3- Energy stored in the capacitor  $C_2$

$$E_{C_2} = (1/2) Q_2 \cdot U_2 = (1/2) \cdot 8 \cdot 4 \Rightarrow E_{C_2} = 16 \mu\text{J}$$



**Exercise 4**

1) The capacity of the two capacitors in parallel,  $C_{23} = C_2 + C_3 = 6 \text{ mF}$  and the capacity of the entire circuit:

$$\frac{1}{C_{ab}} = \frac{1}{C_1} + \frac{1}{C_{23}}$$

$$C_{eq} = 2,0 \text{ mF}$$

2) The charge on the first capacitor is the same as the charge on the whole combination, because it's the only thing to which the left wire is connected. This charge can be found from the capacity.

$$Q_{eq} = Q_1 = C_{eq} \cdot V_{eq} = 12 \text{ mC}$$

There is a charge  $Q_1$  on the opposite side of the first capacitor, which must also come from the next capacitors as they are equal to each other. Therefore,

$$Q_2 = Q_3 = (1/2) Q_1 \\
 Q_1 = 12 \text{ mC}, Q_2 = Q_3 = 6,0 \text{ mC}$$

2) We have  $V_i = Q_i / C_i$  hence  $V_1 = (Q_1/C_1) = 4,0 \text{ V}$

$$\text{And } V_2 = V_3 = (Q_2/C_2) = 2,0 \text{ V}$$

4) the capacity is:

$$C = \frac{Q}{V} = \frac{Q}{Ed} \quad \text{so } C = 2.0 \cdot 10^{-2} \text{ F}$$


5) Energie is :

$$E_p = \frac{1}{2} C U^2 = \frac{1}{2} \cdot Q U \quad \text{so } E_p = 18 \cdot 10^{-9} \text{ J}$$

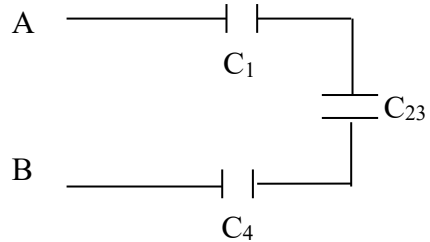**Supplementary exercise 1:**

A 1- Equivalent capacity

$$C_{23} = C_2 + C_3 = 10 + 4 = 14 \mu\text{F} \\
 \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_{23}} + \frac{1}{C_4} = \frac{1}{2} + \frac{1}{14} + \frac{1}{7} = \frac{10}{14} \Rightarrow C_{eq} = 1,4 \mu\text{F}$$



2- Charges carried by capacitors

**In a series connection:  $Q_{AB} = Q_{C1} = Q_{C23} = Q_{C4}$  avec  $Q_{AB} = C_{eq} U_{AB}$   $U_{AB} = U_{C1} + U_{C23} + U_{C4}$**

$$Q_{eq} = C_{eq} U \Rightarrow Q_{eq} = 1,4 \times 12 = 16,8 \mu\text{C} \quad U = U_{AB} = 12 \text{ volt}$$

$$Q_{eq} = Q_{C1} = Q_{C4} = Q_{C23} = 16,8 \mu\text{C}$$

$$\text{And } U_{23} = U_2 = U_3 \Rightarrow \frac{Q_{C23}}{C_{23}} = \frac{Q_{C2}}{C_2} = \frac{Q_{C3}}{C_3}$$



$$\Rightarrow Q_{C_2} = \frac{Q_{C_{23}} \times C_2}{C_{23}} = \frac{16,8 \times 10}{14} = 12 \mu C \text{ and } Q_{C_3} = \frac{Q_{C_{23}} \times C_3}{C_{23}} = \frac{16,8 \times 4}{14} = 4,8 \mu C$$

1- Capacitors voltage

$$U_1 = \frac{Q_{C_1}}{C_1} = \frac{16,8}{2} = 8,4 \text{ Volt} \text{ and } U_4 = \frac{Q_{C_4}}{C_4} = \frac{16,8}{7} = 2,4 \text{ Volt}$$

$$\text{and } U_3 = U_2 = 12 - 8,4 - 2,4 = 1,2 \text{ Volt}$$

B. The capacity of capacitor

$$V = \int E dl = E \int_A^B dl = Ed$$

$$C = \frac{Q}{V} = \frac{Q}{Ed} \text{ so } C = \frac{30 \times 10^{-3}}{100 \times 0,015} = 20 \cdot 10^{-3} F$$

C. The energie is :

$$E_p = \frac{1}{2} CU^2 = \frac{1}{2} \cdot QU \text{ so } E_p = 18 \cdot 10^{-9} J$$

**Supplementary exercise 2:**

1.  $Q_{C_1} = C_1 U_{AD} \Rightarrow U_{AD} = \frac{Q_{C_1}}{C_1} = \frac{10}{4}$   
 $\Rightarrow U_{AD} = 2,5 \text{ Volt}$

2.  $Q_{C_2} = C_2 U_{AD} = 3,5 \times 2,5 = 8,75 \mu C$   
 $Q_{C_3} = C_3 U_{AD} = 2,5 \times 2,5 = 6,25 \mu C$

3.  $U_{BD} = 2 \text{ Volt}$   
 $Q_{C_4} = C_4 U_{BD} = 5 \times 2 = 10 \mu C$

and  $Q_{C_5} = C_5 U_{BD} = 5 \times 2 = 10 \mu C$

4. Let's calculate  $C_{eq}$  :

$$C_{123} = C_1 + C_2 + C_3 = 4 + 3,5 + 2,5 = 10 \mu F$$

$$C_{45} = C_4 + C_5 = 5 + 5 = 10 \mu F$$

$$C_{78} = C_7 + C_8 = 5 + 5 = 10 \mu F$$

$$\frac{1}{C_{eq1}} = \frac{1}{C_{123}} + \frac{1}{C_{45}} = \frac{1}{10} + \frac{1}{10} = \frac{2}{10} \Rightarrow C_{eq1} = 5 \mu F$$

$$\frac{1}{C_{eq2}} = \frac{1}{C_{78}} + \frac{1}{C_6} = \frac{1}{10} + \frac{1}{10} = \frac{2}{10} \Rightarrow C_{eq2} = 5 \mu F$$

$$C_{eq} = C_{eq1} + C_{eq2} = 5 + 5 = 10 \mu F$$

5. Energy stored in the capacitor  $C_1$  :

$$E_{C_1} = \frac{1}{2} C_1 U_{AD}^2 = \frac{1}{2} \cdot 4 \cdot (2,5)^2 = 12,5 \mu J$$

