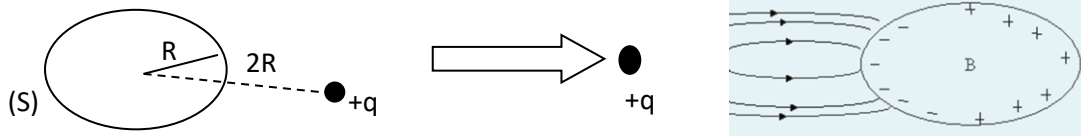




Corrected final exam electricity

Course questions: (6pts)

1. A metal sphere (S) of radius R, initially insulated ($\Delta Q=0$). (1.5pts)



- When (S) is approached with a +q charge, this positive charge attracts the negative charges of the S sphere and repels the positive charges.

The total potential will be : $V' = V_i + V_f = K \frac{Q}{R} + K \frac{+q}{2R}$ (0.5pts)

- When the potential is cancelled (grounding $V=0$), the positive (+) charges of S are neutralized (they flow to ground) and the sphere becomes negatively charged. (0.5pts).

Where : $V'=0$ (0.25pts)

$$\Rightarrow V' = V_i + V_f = K \frac{Q}{R} + K \frac{+q}{2R} = 0$$

$$\Rightarrow Q = -\frac{q}{2} \quad (0.25pts)$$

2. Definition of a capacitor Plane: This is an assembly of two surface-charged planes under total influence. (0.5pts)

Capacitance of a Plan capacitor:

$$C = \frac{Q}{(V_1 - V_2)} = \frac{Q}{U} \quad (0.5pts)$$

The field created by a plane is given by this formula $E = \frac{\sigma}{2\epsilon_0}$.

- The field created by two planes:

$$\vec{E} = \vec{E}_1 + \vec{E}_2 = +\frac{\sigma}{2\epsilon_0} (+\vec{k}) + \frac{-\sigma}{2\epsilon_0} (-\vec{k}) \quad (0.25pts)$$

$$\vec{E} = \frac{\sigma}{\epsilon_0} \vec{k} \quad \text{Coulomb Theoreme} \quad (0.25pts)$$

- Calculating the potential difference:

$$\begin{cases} \vec{E} = -\overrightarrow{grad}V \\ E = E(z) \end{cases} \quad (0.5pts)$$

$$E = -\frac{dV}{dz} \Rightarrow dV = -Edz \quad (0.25pts)$$

$$V_1 - V_2 = \int_0^e Edz = \int_0^e \frac{\sigma}{\epsilon_0} dz = \frac{\sigma}{\epsilon_0} (z_2 - z_1) = \frac{\sigma}{\epsilon_0} e = U \quad (0.25pts)$$

- The capacitance of a spherical capacitor:

$$C = \frac{Q}{(V_1 - V_2)} = \frac{\sigma \cdot S}{\frac{\sigma}{\epsilon_0} e} \quad \text{so} \quad C = \frac{\epsilon_0 S}{e} \quad (0.5pts)$$



3. The current density \vec{j} represents the amount of charge passing through the unit area per unit time (0.5pts). $\vec{j} = \sigma \vec{E}$. (0.5pts)

4. The shape of the elementary electric field $d\vec{E}$ for a linear load distribution is :

$$d\vec{E} = \frac{k dq}{r^2} \vec{u} = k \frac{\lambda dl}{r^2} \vec{u} \quad (0.5pts)$$

Exercise 1: (07 pts)

1- Equivalent capacity :

$$C_{23} = C_2 + C_3 = 10 + 4 = 14 \mu F \quad (0.5pts)$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_{23}} + \frac{1}{C_4} = \frac{1}{2} + \frac{1}{14} + \frac{1}{7} = \frac{10}{14} \Rightarrow C_{eq} = 1,4 \mu F \quad (0.5pts)$$

2- Charges carried by capacitors :

In a series connection:

$$Q_{eq} = Q_{C1} = Q_{C23} = Q_{C4} \quad (0.5pts) \quad \text{with } Q_{eq} = C_{eq} E \text{ et } E = U_{C1} + U_{C23} + U_{C4} \quad (0.5pts)$$

$$Q_{eq} = C_{eq} E \Rightarrow Q_{eq} = 1,4 \times 12 = 16,8 \mu C \quad (0.5pts)$$

$$Q_{eq} = Q_{C1} = Q_{C4} = Q_{C23} = 16,8 \mu C \quad (0.5pts)$$

$$\text{And } U_{23} = U_2 = U_3 \quad (0.5pts) \Rightarrow \frac{Q_{C23}}{C_{23}} = \frac{Q_{C2}}{C_2} = \frac{Q_{C3}}{C_3}$$

$$\Rightarrow Q_{C2} = \frac{Q_{C23} \times C_2}{C_{23}} = \frac{16,8 \times 4}{14} = 4,8 \mu C \quad (0.5pts) \quad \text{and } Q_{C3} = \frac{Q_{C23} \times C_3}{C_{23}} = \frac{16,8 \times 10}{14} = 12 \mu C \quad (0.5pts)$$

3- the ddp of capacitors

$$U_1 = \frac{Q_{C1}}{C_1} = \frac{16,8}{2} = 8,4 \text{ Volt} \quad (0.5pts) \quad \text{and } U_4 = \frac{Q_{C4}}{C_4} = \frac{16,8}{7} = 2,4 \text{ Volt} \quad (0.5pts)$$

$$\text{And } U_3 = U_2 = 12 - 8,4 - 2,4 = 1,2 \text{ Volt} \quad (0.5pts)$$

4. The energy carried by C_1 is:

$$E_p = \frac{1}{2} C U^2 = \frac{1}{2} \cdot Q U \quad (0.5pts) \quad \text{so } E_p = 18 \cdot 10^{-9} J \quad (0.5pts)$$



1- Current intensity I using Kirchoff's laws :


with: $R_1=2\Omega$, $R_2=20\Omega$, $R_3=12\Omega$, $R_4=6\Omega$, $R_5=16\Omega$ and $E=24\text{ V}$

Nods law: $I=I_1+I_2$ (0.5pts)

Lope law:

$E-R_1I-R_2I_1=0$ (0.5pts)

$R_2I_1-R_3I_2-R_4I_2=0$ (0.5pts)

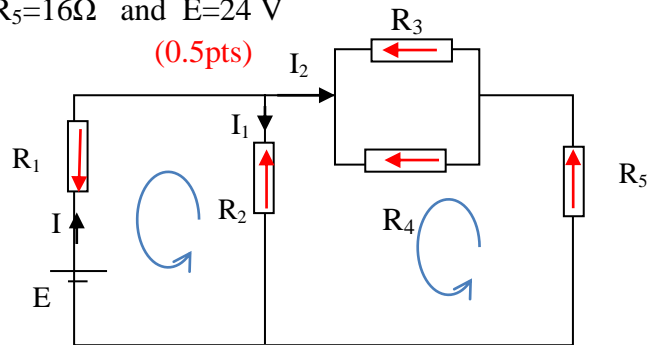

$$\frac{1}{R_{34}} = \frac{1}{R_3} + \frac{1}{R_4} = \frac{1}{6} + \frac{1}{12} = \frac{3}{12} \Rightarrow R_{34} = 4\Omega \text{ (0.5pts)}$$

$$\begin{cases} 24 - 2(I_1 + I_2) - 20 I_1 = 0 \\ 20I_1 - 16I_2 - 4I_2 = 0 \end{cases} \Rightarrow \begin{cases} 12 - 2I_2 - 22I_1 = 0 \\ 20I_1 - 20I_2 = 0 \end{cases}$$

$I_2=I_1$ so $24-24I_2=0$ then $I_2=I_1=1\text{ A}$ (0.5pts) and $I=2\text{A}$ (0.5pts)

2- The current I using the equivalent resistance:

$R_{345}=16+4=20\ \Omega$ (0.25pts) ,

$$\frac{1}{R_{2345}} = \frac{1}{R_2} + \frac{1}{R_{345}} \text{ (0.25pts)} = \frac{1}{20} + \frac{1}{20} = \frac{2}{20} \Rightarrow R_{2345} = 10\ \Omega \text{ (0.25pts)}$$

$R_{eq}=R_1+R_{2345}$ (0.25pts) $=2+10=12\ \Omega$ with $E-R_{eq}I_1=0$ (0.5pts)

$$\text{so } I_1 = \frac{E}{R_{eq}} = \frac{24}{12} = 2\text{ A} \text{ (0.5pts)}$$

3- Circulating currents in resistors R_3 and R_4 :

$U_{34}=R_{34}I_2=4 \times 1=4\text{V}$ (0.25pts) with $U_{34} = U_3 = U_4 \Rightarrow U_{34} = R_3 I'_2 = R_4 I''_2$ (0.25pts)

So $I'_2 = \frac{U_{34}}{R_3} = \frac{4}{12} = \frac{1}{3}\text{ A}$ (0.25pts) and $I''_2 = \frac{U_{34}}{R_4} = \frac{4}{6} = \frac{2}{3}\text{ A}$ (0.25pts)

4- we have $P_T = U \cdot I = R_{eq} \cdot I^2 = 12 \cdot 4 = 48\text{ W}$ (0.5pts)

In the other hand: $P = EI = 24\text{V} \times 2\text{A} = 48\text{W}$ (0.5pts)

Conclusion: $P_T = P$ (0.5pts)